

Development of general purpose low-power small-area 10 bit CMOS DAC


Dominik Przyborowski

April 1, 2009

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

DAC Architecture Overview

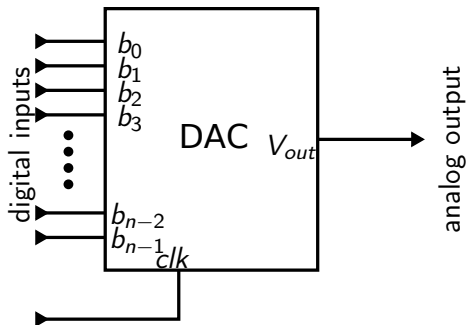

Block diagram of digital-to-analog converter.

$$V_{out} = \sum_{k=0}^{n-1} b_k \cdot 2^k \cdot S_{ref},$$

S_{ref} – reference value (voltage, current or charge).

DAC Architecture Overview

Nyquist rate DACs architectures:

- charge division,
- resistor strings,
- voltage mode R-2R ladder,
- current mode R-2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Nyquist rate DACs architectures:

- charge division,
- resistor strings,
- voltage mode R-2R ladder,
- current mode R-2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Nyquist rate DACs architectures:

- charge division,
- resistor strings,
- voltage mode R-2R ladder,
- current mode R-2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Nyquist rate DACs architectures:

- charge division,
- resistor strings,
- voltage mode R–2R ladder,
- current mode R–2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Nyquist rate DACs architectures:

- charge division,
- resistor strings,
- voltage mode R-2R ladder,
- current mode R-2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Nyquist rate DACs architectures:

- charge division,
- resistor strings,
- voltage mode R–2R ladder,
- current mode R–2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Nyquist rate DACs architectures:


- charge division,
- resistor strings,
- voltage mode R-2R ladder,
- current mode R-2R ladder,
- current steering.

Oversampling DACs:

- $\Sigma - \Delta$ modulators – not discussed here.

DAC Architecture Overview

Charge Division.

 

4 bit binary-weighted capacitor DAC.

Properties

$$V_{out} = -\frac{C}{C_f} \cdot \sum_{k=0}^{N-1} 2^k \cdot S_k \cdot V_{ref}$$


Resolution up to 12 bits

Low DC power consumption (only Op Amp and digital part)

Simple layout (only capacitors and switches)

DAC Architecture Overview

Charge Division.

 

4 bit binary-weighted capacitor DAC.


Properties

$$V_{out} = -\frac{C}{C_f} \cdot \sum_{k=0}^{N-1} 2^k \cdot S_k \cdot V_{ref}$$

- resolution up to 12 bits,
- low DC power consumption (only Op Amp and digital part)
- requires refreshing (capacitors leakage current is $\approx 1\text{aA}$)

DAC Architecture Overview

Charge Division.

 

4 bit binary-weighted capacitor DAC.


Properties

$$V_{out} = -\frac{C}{C_f} \cdot \sum_{k=0}^{N-1} 2^k \cdot S_k \cdot V_{ref}$$

- resolution up to 12 bits,
- low DC power consumption (only Op Amp and digital part)
- requires refreshing (capacitors leakage current is $\approx 1\text{aA}$)

DAC Architecture Overview

Charge Division.

 

4 bit binary-weighted capacitor DAC.


Properties

$$V_{out} = -\frac{C}{C_f} \cdot \sum_{k=0}^{N-1} 2^k \cdot S_k \cdot V_{ref}$$

- resolution up to 12 bits,
- low DC power consumption (only Op Amp and digital part)
- requires refreshing (capacitors leakage current is $\approx 1\text{aA}$)

DAC Architecture Overview

Resistor String.

 

3 bit resistor string DAC.

Properties


$$V_{out} = \frac{\sum_{k=0}^{N-1} S_k \cdot 2^k}{2^N} \cdot V_{ref}$$

Requires rail-to-rail Op Amp.

Requires many bits of digital code.

DAC Architecture Overview

Resistor String.

 

3 bit resistor string DAC.


Properties

$$V_{out} = \frac{\sum_{k=0}^{N-1} S_k \cdot 2^k}{2^N} \cdot V_{ref}$$

- Requires rail-to-rail Op Amp.
- Requires *binary* $\rightarrow 1$ from N decoder.

DAC Architecture Overview

Resistor String.

 

3 bit resistor string DAC.


Properties

$$V_{out} = \frac{\sum_{k=0}^{N-1} S_k \cdot 2^k}{2^N} \cdot V_{ref}$$


- Requires rail-to-rail Op Amp.
- Requires *binary* \rightarrow 1 from N decoder.

DAC Architecture Overview

Resistor R-2R Ladder.

 

a) Voltage mode

 


b) Current mode

$$V_{out} = \left(1 + \frac{R_f}{R_1}\right) \cdot \sum_{k=1}^N \frac{S_{N-k} \cdot V_{ref}}{2^k}$$

$$V_{out} = \frac{V_{ref}}{2} \left[1 + \frac{R_f}{R} \left(\sum_{k=1}^N \frac{S_{N-k}}{2^{N-k}} - 1\right)\right]$$

DAC Architecture Overview

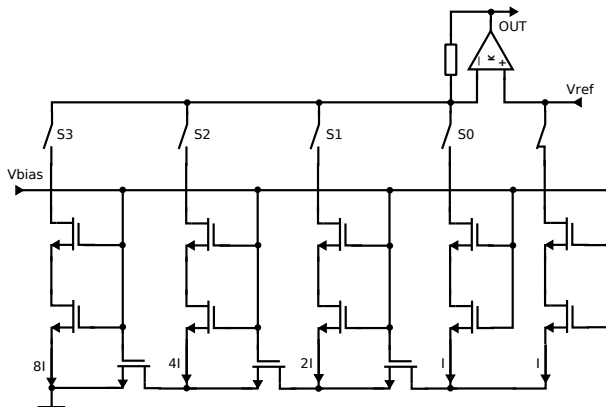
Resistor R-2R Ladder – MOS implementation I.



4 bit L-2L MOS Ladder DAC.

DAC Architecture Overview

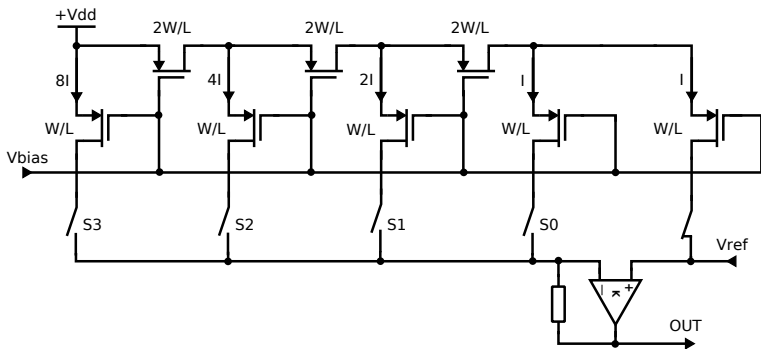Resistor R-2R Ladder – MOS implementation II.



4 bit W-2W MOS Ladder DAC.

DAC Architecture Overview

Resistor R-2R Ladder – MOS implementation III.

M-2M mismatch considerations

- In M-2M network transistors in different operational points.
- Matching in saturation region is determined by overdrive voltage:

$$\sigma(I_d) = \sqrt{\frac{A_\beta^2}{W \cdot L} + \left(\frac{2 \cdot 100\% \cdot A_{V_{th}}}{V_{ov}}\right)^2 \cdot \frac{1}{W \cdot L}}$$


- Matching of MOS transistors in triode region is affected by output opamp offset:

$$\sigma(I_d) = \sqrt{\frac{A_\beta^2}{W \cdot L} + \left(\frac{100\% \cdot A_{V_{th}}}{V_{ov} - \frac{1}{2}V_{ds}}\right)^2 \cdot \frac{1}{W \cdot L} + \left(100\% \cdot \frac{\Delta V_{ds}}{V_{ds}}\right)^2}$$

- Simulations results required *special care* – problem with discontinuities of the BSIM transistors model.

DAC Architecture Overview

Current Steering.

 

4 bit Current Steering DAC.

$$V_{out} = I_{ref} \cdot R \cdot \sum_{K=0}^{N-1} S_k \cdot 2^k$$

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

10 bit Low-Power Small-Area Current-Steering DAC design. Specification

Requirements:

- 10 bit resolution.
- High swing voltage output.
- Low power consumption – below 1 [mW].
- Small area.

Considered architectures:

- Current steering.
- Resistors ladder.

Chosen architecture:

- Current steering – matching of MOS better than resistors.

10 bit Low-Power Small-Area Current-Steering DAC design. Specification

Requirements:

- 10 bit resolution.
- High swing voltage output.
- Low power consumption – below 1 [mW].
- Small area.

Considered architectures:

- Current steering.
- Resistors ladder.

Chosen architecture:

- Current steering – matching of MOS better than resistors.

10 bit Low-Power Small-Area Current-Steering DAC design. Specification

Requirements:

- 10 bit resolution.
- High swing voltage output.
- Low power consumption – below 1 [mW].
- Small area.

Considered architectures:

- Current steering.
- Resistors ladder.

Chosen architecture:

- Current steering – matching of MOS better than resistors.

10 bit Low-Power Small-Area Current-Steering DAC design. Specification

Requirements:

- 10 bit resolution.
- High swing voltage output.
- Low power consumption – below 1 [mW].
- Small area.

Considered architectures:

- Current steering.
- Resistors ladder.


Chosen architecture:

- Current steering – matching of MOS better than resistors.

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - **Circuit Design.**
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

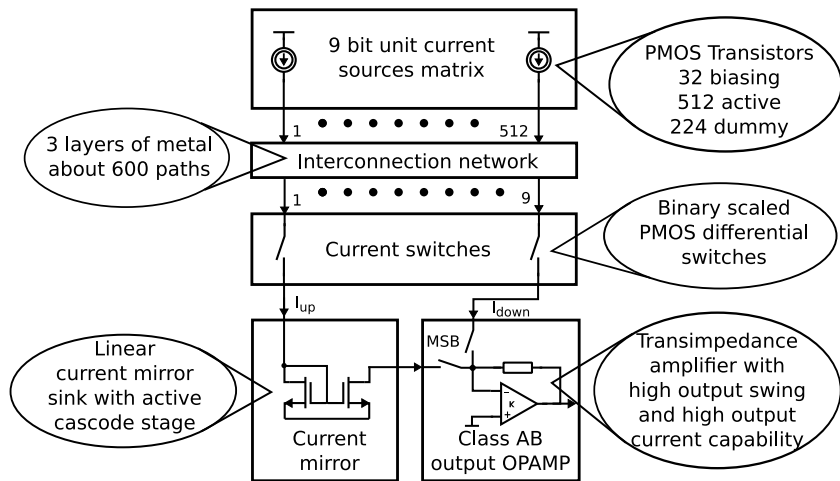10 bit Low-Power Small-Area Current-Steering DAC design. Circuit Design.



Block diagram of proposed DAC.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array I.

Require for 9 bit resolution:

$$\delta I_{MSB} \leq \frac{1}{3} \cdot 2^{-9} \cdot 100\% = 0.065\%$$

Formulas for calculating dimensions:

$$\frac{W}{L} = \frac{2 \cdot I_D}{\beta \cdot V_{ov}^2}, \quad \beta = \mu_0 \cdot C_{ox}$$

$$W \cdot L \geq \frac{1}{\sigma^2(I_D)} \cdot \left[A_\beta^2 + \left(\frac{2 \cdot A_{V_{th}}}{V_{ov}} \cdot 100\% \right)^2 \right]$$

Mismatch parameters in used technology:

NMOS:	$A_\beta = 0.2 [\mu m \cdot \%]$	$A_{V_{th}} = 8.2 [\mu m \cdot mV]$
PMOS:	$A_\beta = 0.4 [\mu m \cdot \%]$	$A_{V_{th}} = 14.9 [\mu m \cdot mV]$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array I.

Require for 9 bit resolution:

$$\delta I_{MSB} \leq \frac{1}{3} \cdot 2^{-9} \cdot 100\% = 0.065\%$$

Formulas for calculating dimensions:

$$\frac{W}{L} = \frac{2 \cdot I_D}{\beta \cdot V_{ov}^2}, \quad \beta = \mu_0 \cdot C_{ox}$$

$$W \cdot L \geq \frac{1}{\sigma^2(I_D)} \cdot \left[A_\beta^2 + \left(\frac{2 \cdot A_{V_{th}}}{V_{ov}} \cdot 100\% \right)^2 \right]$$

Mismatch parameters in used technology:

$$\text{NMOS: } A_\beta = 0.2 [\mu m \cdot \%] \quad A_{V_{th}} = 8.2 [\mu m \cdot mV]$$

$$\text{PMOS: } A_\beta = 0.4 [\mu m \cdot \%] \quad A_{V_{th}} = 14.9 [\mu m \cdot mV]$$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array I.

Require for 9 bit resolution:

$$\delta I_{MSB} \leq \frac{1}{3} \cdot 2^{-9} \cdot 100\% = 0.065\%$$

Formulas for calculating dimensions:

$$\frac{W}{L} = \frac{2 \cdot I_D}{\beta \cdot V_{ov}^2}, \quad \beta = \mu_0 \cdot C_{ox}$$

$$W \cdot L \geq \frac{1}{\sigma^2(I_D)} \cdot \left[A_\beta^2 + \left(\frac{2 \cdot A_{V_{th}}}{V_{ov}} \cdot 100\% \right)^2 \right]$$

Mismatch parameters in used technology:

NMOS:	$A_\beta = 0.2 [\mu m \cdot \%]$	$A_{V_{th}} = 8.2 [\mu m \cdot mV]$
PMOS:	$A_\beta = 0.4 [\mu m \cdot \%]$	$A_{V_{th}} = 14.9 [\mu m \cdot mV]$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array II.

Choice of transistors size:

- Assumed LSB current = $100[nA]$
- Assumed current source overdrive voltage $\geq 500[mV]$
- Chosen transistor type – PMOS
- Chosen W/L unit transistor ratio – $1/80$ ($V_{ov} = 637[mV]$)
- Calculated unit current source dimensions – $0.5\mu/40\mu$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array II.

Choice of transistors size:

- Assumed LSB current = $100[nA]$
- Assumed current source overdrive voltage $\geq 500[mV]$
- Chosen transistor type – PMOS
- Chosen W/L unit transistor ratio – $1/80$ ($V_{ov} = 637[mV]$)
- Calculated unit current source dimensions – $0.5\mu/40\mu$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array II.

Choice of transistors size:

- Assumed LSB current = $100[nA]$
- Assumed current source overdrive voltage $\geq 500[mV]$
- Chosen transistor type – PMOS
- Chosen W/L unit transistor ratio – $1/80$ ($V_{ov} = 637[mV]$)
- Calculated unit current source dimensions – $0.5\mu/40\mu$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array II.

Choice of transistors size:

- Assumed LSB current = $100[nA]$
- Assumed current source overdrive voltage $\geq 500[mV]$
- Chosen transistor type – PMOS
- Chosen W/L unit transistor ratio – $1/80$ ($V_{ov} = 637[mV]$)
- Calculated unit current source dimensions – $0.5\mu/40\mu$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – 9 bit Current Sources Array II.

Choice of transistors size:

- Assumed LSB current = $100[nA]$
- Assumed current source overdrive voltage $\geq 500[mV]$
- Chosen transistor type – PMOS
- Chosen W/L unit transistor ratio – $1/80$ ($V_{ov} = 637[mV]$)
- Calculated unit current source dimensions – $0.5\mu/40\mu$

10 bit Low-Power Small-Area Current-Steering DAC design.


Circuit Design – 9 bit Current Sources Array II.

Choice of transistors size:


- Assumed LSB current = $100[nA]$
- Assumed current source overdrive voltage $\geq 500[mV]$
- Chosen transistor type – PMOS
- Chosen W/L unit transistor ratio – $1/80$ ($V_{ov} = 637[mV]$)
- Calculated unit current source dimensions – $0.5\mu/40\mu$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Current Switches.

 

a) unary (best matching)

 

b) binary (lowest area)


Current switches – conclusion

To minimize area binary switching (b) was chosen.


Dimensions of LSB switch – $0.4\mu/0.35\mu$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Current Switches.

 

a) unary (best matching)

 


b) binary (lowest area)

Current switches – conclusion

To minimize area binary switching (b) was chosen.
 Dimensions of LSB switch – $0.4\mu/0.35\mu$.

10 bit Low-Power Small-Area Current-Steering DAC design.

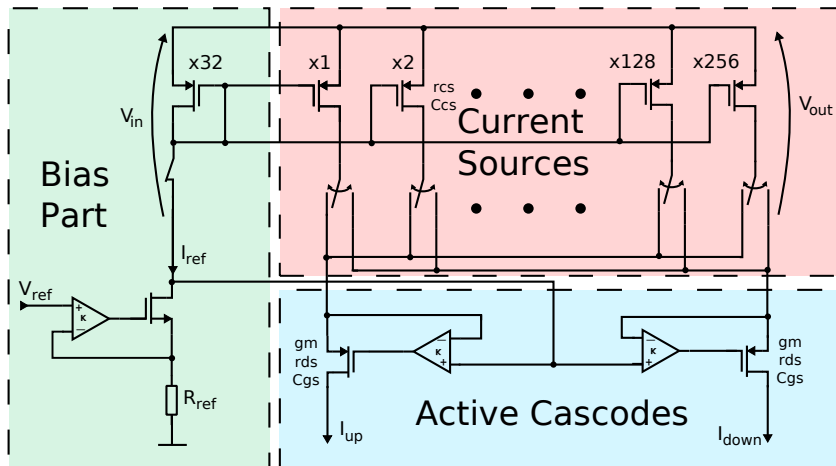Circuit Design – Current Source Array with Active Cascodes Stage.



Bias circuit, current sources array and active cascode stage.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Active Cascode Stage.

Advantages of active cascodes:

- Drain current independent from channel modulation factor.
- Strongly increases output resistance:

$$r_{out} \simeq K \cdot g_m \cdot r_{ds} \cdot r_{CS} \approx 10^{14} \div 10^{16} \Omega$$

- Glitch reduction.

Possibles problems:

- Stability

dominant pole	nondominant pole
p_1 of OTA	$\frac{g_m}{C_{gs} + \frac{C_{CS}}{K}}$

Needs minimum current!

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Active Cascode Stage.

Advantages of active cascodes:

- Drain current independent from channel modulation factor.
- Strongly increases output resistance:

$$r_{out} \simeq K \cdot g_m \cdot r_{ds} \cdot r_{CS} \approx 10^{14} \div 10^{16} \Omega$$

- Glitch reduction.

Possibles problems:

- Stability

dominant pole	nondominant pole
p_1 of OTA	$\frac{g_m}{C_{gs} + \frac{C_{CS}}{K}}$

Needs minimum current!

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Active Cascode Stage.

Advantages of active cascodes:

- Drain current independent from channel modulation factor.
- Strongly increases output resistance:

$$r_{out} \simeq K \cdot g_m \cdot r_{ds} \cdot r_{CS} \approx 10^{14} \div 10^{16} \Omega$$

- Glitch reduction.

Possibles problems:

- Stability

dominant pole	nondominant pole
p_1 of OTA	$\frac{g_m}{C_{gs} + \frac{C_{CS}}{K}}$

Needs minimum current!

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Active Cascode Stage.

Advantages of active cascodes:

- Drain current independent from channel modulation factor.
- Strongly increases output resistance:

$$r_{out} \simeq K \cdot g_m \cdot r_{ds} \cdot r_{CS} \approx 10^{14} \div 10^{16} \Omega$$

- Glitch reduction.

Possibles problems:

- Stability

dominant pole	nondominant pole
p_1 of OTA	$\frac{g_m}{C_{gs} + \frac{C_{CS}}{K}}$

Needs minimum current!

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Active Cascode Stage.

Advantages of active cascodes:

- Drain current independent from channel modulation factor.
- Strongly increases output resistance:

$$r_{out} \simeq K \cdot g_m \cdot r_{ds} \cdot r_{CS} \approx 10^{14} \div 10^{16} \Omega$$

- Glitch reduction.

Possible problems:

- Stability

dominant pole	nondominant pole
p_1 of OTA	$\frac{g_m}{C_{gs} + \frac{C_{CS}}{K}}$

Needs minimum current!

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Active Cascode Stage.

Advantages of active cascodes:

- Drain current independent from channel modulation factor.
- Strongly increases output resistance:

$$r_{out} \simeq K \cdot g_m \cdot r_{ds} \cdot r_{CS} \approx 10^{14} \div 10^{16} \Omega$$

- Glitch reduction.

Possibles problems:


- Stability

dominant pole	nondominant pole
p_1 of OTA	$\frac{g_m}{C_{gs} + \frac{C_{CS}}{K}}$

Needs minimum current!

10 bit Low-Power Small-Area Current-Steering DAC design.

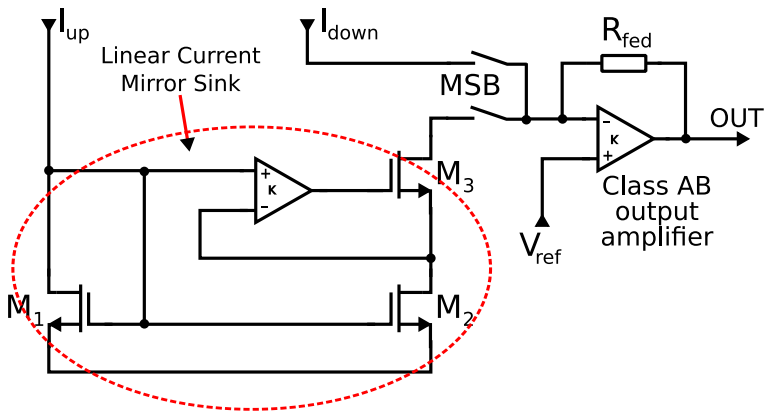Circuit Design – High Swing Output Stage (Including Current Mirror Sink) I.



$$\frac{W_1}{L_1} = \frac{W_2}{L_2} = 16 \cdot \frac{3.2\mu}{52.5\mu}$$

High swing output circuit.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – High Swing Output Stage II.

Relation between I_{down} and I_{up} :

$$I_{down} = 511 \cdot I_{LSB} - B_{dec} \cdot I_{up}$$

B_{dec} – decimal representation of input word (without MSB bit).

Output voltage:

- MSB = 0: $V_{out} = V_{ref} - (511 - B_{dec}) \cdot I_{LSB} \cdot R_{fed}$
- MSB = 1: $V_{out} = V_{ref} + B_{dec} \cdot I_{LSB} \cdot R_{fed}$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – High Swing Output Stage II.

Relation between I_{down} and I_{up} :

$$I_{down} = 511 \cdot I_{LSB} - B_{dec} \cdot I_{up}$$

B_{dec} – decimal representation of input word (without MSB bit).

Output voltage:

- MSB = 0: $V_{out} = V_{ref} - (511 - B_{dec}) \cdot I_{LSB} \cdot R_{fed}$
- MSB = 1: $V_{out} = V_{ref} + B_{dec} \cdot I_{LSB} \cdot R_{fed}$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – High Swing Output Stage II.

Relation between I_{down} and I_{up} :

$$I_{down} = 511 \cdot I_{LSB} - B_{dec} \cdot I_{up}$$

B_{dec} – decimal representation of input word (without MSB bit).

Output voltage:

- MSB = 0: $V_{out} = V_{ref} - (511 - B_{dec}) \cdot I_{LSB} \cdot R_{fed}$
- MSB = 1: $V_{out} = V_{ref} + B_{dec} \cdot I_{LSB} \cdot R_{fed}$

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Single Stage OTAs.

Two types of amplifiers were used:

- Single stage OTAs in active cascode stages and biasing. Depending on voltage level OTA use either NMOS or PMOS input differential pair.
- Two stage class AB operational amplifier for output current-to-voltage converter.

Single stage OTA – details:

- Architecture – folded cascode.
- Power consumption [μW] – 3.5 (NMOS), 25 (PMOS).
- Open loop Gain [dB] – 60 (NMOS), 88 (PMOS).
- Gain x Bandwidth (GBW) [MHz] – 1 (NMOS), 7 (PMOS).
- Phase Margin $> 70^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Single Stage OTAs.

Two types of amplifiers were used:

- Single stage OTAs in active cascode stages and biasing. Depending on voltage level OTA use either NMOS or PMOS input differential pair.
- Two stage class AB operational amplifier for output current-to-voltage converter.

Single stage OTA – details:

- Architecture – folded cascode.
- Power consumption [μW] – 3.5 (NMOS), 25 (PMOS).
- Open loop Gain [dB] – 60 (NMOS), 88 (PMOS).
- Gain x Bandwidth (GBW) [MHz] – 1 (NMOS), 7 (PMOS).
- Phase Margin $> 70^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Single Stage OTAs.

Two types of amplifiers were used:

- Single stage OTAs in active cascode stages and biasing. Depending on voltage level OTA use either NMOS or PMOS input differential pair.
- Two stage class AB operational amplifier for output current-to-voltage converter.

Single stage OTA – details:

- Architecture – folded cascode.
- Power consumption [μW] – 3.5 (NMOS), 25 (PMOS).
- Open loop Gain [dB] – 60 (NMOS), 88 (PMOS).
- Gain x Bandwidth (GBW) [MHz] – 1 (NMOS), 7 (PMOS).
- Phase Margin $> 70^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Single Stage OTAs.

Two types of amplifiers were used:

- Single stage OTAs in active cascode stages and biasing. Depending on voltage level OTA use either NMOS or PMOS input differential pair.
- Two stage class AB operational amplifier for output current-to-voltage converter.

Single stage OTA – details:

- Architecture – folded cascode.
- Power consumption [μW] – 3.5 (NMOS), 25 (PMOS).
- Open loop Gain [dB] – 60 (NMOS), 88 (PMOS).
- Gain x Bandwidth (GBW) [MHz] – 1 (NMOS), 7 (PMOS).
- Phase Margin $> 70^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Single Stage OTAs.

Two types of amplifiers were used:


- Single stage OTAs in active cascode stages and biasing. Depending on voltage level OTA use either NMOS or PMOS input differential pair.
- Two stage class AB operational amplifier for output current-to-voltage converter.

Single stage OTA – details:

- Architecture – folded cascode.
- Power consumption [μW] – 3.5 (NMOS), 25 (PMOS).
- Open loop Gain [dB] – 60 (NMOS), 88 (PMOS).
- Gain \times Bandwidth (GBW) [MHz] – 1 (NMOS), 7 (PMOS).
- Phase Margin $> 70^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

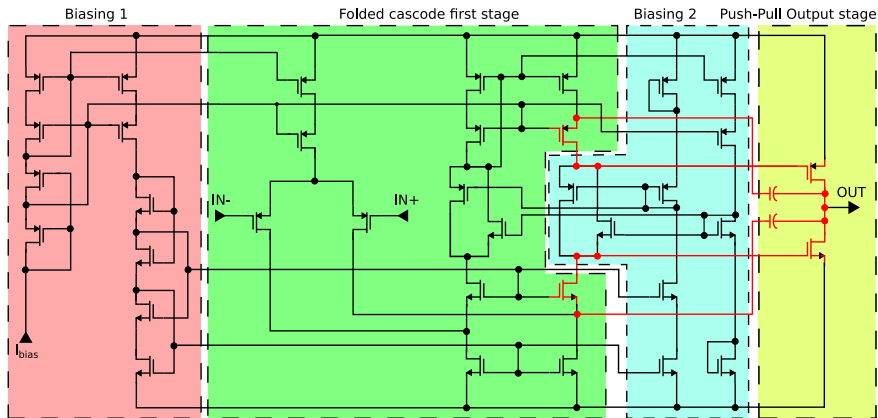Circuit Design – Class AB Operational Amplifier I.



Schematic of output class AB operational amplifier.

— Cascoded Miller compensation.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2-3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2-3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2-3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2-3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2-3 times smaller comp. cap. (wider bandwidth)
- ✓ Doesn't require resistor
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2–3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2–3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2–3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier II.

Class AB OP-AMP:

- *Sooch* cascode current mirror used for biasing.
- 1st stage build as a folded cascode.
- Bias of Push-Pull output stage designed as *floating current source*.
- Push-Pull output stage with **cascode Miller compensation technique**.

Cascode Miller compensation technique pros and cons:

- ✓ Better PSRR (Power Supply Rejection Ratio).
- ✓ Needs 2–3 times smaller comp. cap. (wider bandwidth).
- ✓ Doesn't require resistor.
- ✗ Complicated transfer function – 3 poles and 2 zeros (problems with high frequency gain peak).

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier III.

Class AB OP-AMP parameters:

- Power consumption – $65 \mu W (+V_{dd} \cdot I_{out})$.
- Open loop gain – 115 dB (for zero current load)
- GBW – 2 MHz
- Phase Margin $> 75^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier III.

Class AB OP-AMP parameters:

- Power consumption – $65 \mu W (+V_{dd} \cdot I_{out})$.
- Open loop gain – 115 dB (for zero current load)
- GBW – 2 MHz
- Phase Margin $> 75^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier III.

Class AB OP-AMP parameters:

- Power consumption – $65 \mu W (+V_{dd} \cdot I_{out})$.
- Open loop gain – 115 dB (for zero current load)
- GBW – 2 MHz
- Phase Margin $> 75^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier III.

Class AB OP-AMP parameters:

- Power consumption – $65 \mu W (+V_{dd} \cdot I_{out})$.
- Open loop gain – 115 dB (for zero current load)
- GBW – 2 MHz
- Phase Margin $> 75^\circ$.

10 bit Low-Power Small-Area Current-Steering DAC design.

Circuit Design – Class AB Operational Amplifier III.

Class AB OP-AMP parameters:


- Power consumption – $65 \mu W (+V_{dd} \cdot I_{out})$.
- Open loop gain – 115 dB (for zero current load)
- GBW – 2 MHz
- Phase Margin $> 75^\circ$.

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

Layout


9 bit Current Sources Array.

 

Block Diagram of DAC Matrix Layout.

Layout

DAC Core.

 


Layout of 1st prototype (295x595 μ m).

Outline


- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

1st Prototype Measurements Results

Static Measurements I.

 

DAC transfer curve

 

Integral (INL) and differential (DNL) nonlinearities.

1st Prototype Measurements Results

Static Measurements II.


1 st chip	Channel no	1	2	3	4	5
	LSB value [mV]	2.62	2.59	2.62	2.64	2.68
	max. INL [LSB]	0.65	0.75	0.6	0.6	0.65
	max. DNL [LSB]	1.1	0.9	1.1	0.9	1.05
	Codes of DNL > 0.5	13	17	14	8	26
	Nr of missing values	4	0	2	0	3
2 nd chip	Channel no	1	2	3	4	5
	LSB value [mV]	2.58	2.59	2.62	2.61	2.63
	max. INL [LSB]	0.45	0.5	0.6	0.6	0.7
	max. DNL [LSB]	0.75	0.95	0.8	0.7	1.2
	Codes of DNL > 0.5	15	2	29	22	20
	Nr of missing values	0	2	0	0	2

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 **1st Prototype Measurements Results**
 - Static Measurements
 - **Power Measurements**
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

1st Prototype Measurements Results

Power Measurements

 


Relation between power consumption and DAC input code.

Outline


- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - **Transient Measurements**
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

1st Prototype Measurements Results

Transient Measurements.

 

Waveform showing 1 LSB steps.

 

Worst case settling time (between first and last input code).

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

Comparison with other low-power 10 bit DACs

	1	2	3	4	This work
architecture	current steering	R-2R ladder	resistor ladder	resistor string	current steering
technology	0.35 μm CMOS	0.18 μm CMOS	0.35 μm CMOS	0.13 μm CMOS	0.35 μm CMOS
power cons. [mW]	≤ 7.8	4	0.07 (analog part)	0.5	≤ 0.6
area [mm ²]	0.23	0.01	0.022	0.18	0.18
max INL [LSB]	0.2	0.75	0.7	2.0	0.6
max DNL [LSB]	0.2	0.7	0.35	0.5	0.8
speed	upd. rate 30 MS/s	low frequency	set. time 3 $\mu\text{s}/10\text{pF}$	upd. rate 2MS/s	worst t_{set} 2 μs 1 LSB t_r < 500 ns
output type	current $\leq 2.5\text{mA}$	current < 2.2mA	voltage without buffer	voltage high-swing	voltage high-swing

- 1 M. Borremans, A. Van den Bosch, M. Steyeart, W. Sansen, *A low power 10-bit CMOS D/A converter for high speed applications*, IEEE 2001 custom integrated circuits conference.
- 2 B. Greenlay, R. Veith, Dong-Young Chang, Un-Ku Moon, *A low-voltage 10-bit CMOS DAC in 0.01-mm² die area*, IEEE Transactions on Circuits and Systems, vol. 52, no 5, 2005.
- 3 Y. Perelman, R. Ginosar, *A low-power inverted ladder D/A converter*, IEEE Transactions on Circuits and Systems, vol. 53, no 6, 2006.
- 4 F. Ge, M. Trivedi, B. Thomas, W. Jiang, H. Song, *1.5V 0.5mW 2MSPS 10B DAC with rail-to-rail output in 0.13 μm CMOS technology*, SOC Conference, 2008 IEEE International.

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

Possible Improvements.

What is not good:

- DNL higher than expected (over 0.5 LSB).
Some missing values.
- Asymmetry of rise time for outputs signals input code with $MSB = 1$ and $MSB = 0$.

Solutions:

- Layout of current source matrix to be improved.
- Large time constant of linear current mirror sink.

Possible Improvements.

What is not good:

- DNL higher than expected (over 0.5 LSB).
Some missing values.
- Asymmetry of rise time for outputs signals input code with $MSB = 1$ and $MSB = 0$.

Solutions:

- Layout of current source matrix to be improved.
- Large time constant of linear current mirror sink.

Possible Improvements.

What is not good:

- DNL higher than expected (over 0.5 LSB).
Some missing values.
- Asymmetry of rise time for outputs signals input code with $MSB = 1$ and $MSB = 0$.

Solutions:

- Layout of current source matrix to be improved.
- Large time constant of linear current mirror sink.

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.

Design of 2nd prototype – Improvements.

Circuit improvements:

- New layout of the current sources matrix.
- Small improvements in amplifiers design.
- Decreased dimensions of linear current mirror sink and adds trimming.

Parameters of amplifiers in 2nd prototype:

	OTA N	OTA P	OP-AMP
Gain [dB]	96	93	136
GBW [Hz] (10pF load)	65k	130k	3M
PM [°] (10pF load)	96	90	70
Total power cons. [μ W]	5	10	72.5

Design of 2nd prototype – Improvements.

Circuit improvements:

- New layout of the current sources matrix.
- Small improvements in amplifiers design.
- Decreased dimensions of linear current mirror sink and adds trimming.

Parameters of amplifiers in 2nd prototype:

	OTA N	OTA P	OP-AMP
Gain [dB]	96	93	136
GBW [Hz] (10pF load)	65k	130k	3M
PM [°] (10pF load)	96	90	70
Total power cons. [μ W]	5	10	72.5

Design of 2nd prototype – Improvements.

Circuit improvements:

- New layout of the current sources matrix.
- Small improvements in amplifiers design.
- Decreased dimensions of linear current mirror sink and adds trimming.

Parameters of amplifiers in 2nd prototype:

	OTA N	OTA P	OP-AMP
Gain [dB]	96	93	136
GBW [Hz] (10pF load)	65k	130k	3M
PM [°] (10pF load)	96	90	70
Total power cons. [μ W]	5	10	72.5

Design of 2nd prototype – Improvements.

Circuit improvements:

- New layout of the current sources matrix.
- Small improvements in amplifiers design.
- Decreased dimensions of linear current mirror sink and adds trimming.

Parameters of amplifiers in 2nd prototype:


	OTA N	OTA P	OP-AMP
Gain [dB]	96	93	136
GBW [Hz] (10pF load)	65k	130k	3M
PM [°] (10pF load)	96	90	70
Total power cons. [μ W]	5	10	72.5

Outline

- 1 DAC Architecture Overview
- 2 10 bit Low-Power Small-Area Current-Steering DAC design.
 - Specification
 - Circuit Design.
 - Layout
- 3 1st Prototype Measurements Results
 - Static Measurements
 - Power Measurements
 - Transient Measurements
 - Comparison with other low-power 10 bit DACs
 - Possible Improvements.
- 4 Design of 2nd prototype – Improvements.
 - Circuit.
 - Layout.


Layout of 2nd prototype – Improvements.

9 bit Current Sources Array.

 

Block Diagram of DAC Matrix Layout.

 Layout of 2nd prototype – Improvements. DAC Core.



Layout of 2nd prototype (385x530 μ m).

Summary

- 1st prototype of 10 bit DAC is fully functional.
- Measurements results are generally in good agreement with simulations:
 - Transfer curve – $\text{LSB} \simeq 2.6 \text{ [mV]}$
 - Integral Non-Linearity (INL) $\simeq 0.6 \text{ [LSB]}$
 - Differential Non-Linearity (DNL) $\simeq 0.8 \text{ [LSB]}$
 - Full scale settling time = 2 [\mu s]
 - 1 LSB settling time $< 500 \text{ [ns]}$.
- Differential non-linearity is slightly higher than expected – attributed to CS matrix layout.
- Improved design is completed and ready for submission.