

# Investigation of M – 2M and Exponential Digital-to-Analog Converters

Dominik Przyborowski

Department of Particle Interactions and Detection Techniques  
Nuclear Electronics and Radiation Detection Group

May 10, 2010

# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion

# Outline

- 1 8 bits M-2M DAC
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion

# 8 bits M-2M DACs

## Goals of Design

### Goals of Design

- Static 8 bits DAC
- Low power consumption  $< 100 \mu W$
- Small core size  $< 0.05 \text{ mm}^2$

### Destination

Fine adjustment of voltages in every channel

### Proposed architecture

M-2M Ladder

- Small number of elements  $(4N+1)$
- Simple layout

# 8 bits M-2M DACs

## Goals of Design

### Goals of Design

- Static 8 bits DAC
- Low power consumption  $< 100 \mu W$
- Small core size  $< 0.05 \text{ mm}^2$

### Destination

Fine adjustment of voltages in every channel

### Proposed architecture

M-2M Ladder

- Small number of elements  $(4N+1)$
- Simple layout

# 8 bits M-2M DACs

## Goals of Design

### Goals of Design

- Static 8 bits DAC
- Low power consumption  $< 100 \mu W$
- Small core size  $< 0.05 \text{ mm}^2$

### Destination

Fine adjustment of voltages in every channel

### Proposed architecture

M-2M Ladder

- Small number of elements  $(4N+1)$
- Simple layout

# 8 bits M-2M DACs

## Goals of Design

### Goals of Design

- Static 8 bits DAC
- Low power consumption  $< 100 \mu W$
- Small core size  $< 0.05 \text{ mm}^2$

### Destination

Fine adjustment of voltages in every channel

### Proposed architecture

M-2M Ladder

- Small number of elements  $(4N+1)$
- Simple layout

# Outline


- 1 8 bits M-2M DAC
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion



# 8 bits M-2M DACs

## Principle of Operation

### MOS transistor equivalent circuit

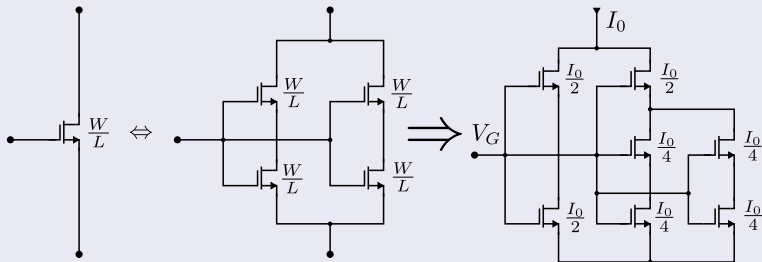

Current flowing into series-parallel identically designed transistors is equally divided between them

# Outline

- 1 8 bits M-2M DAC
  - Goals of Design
  - Principle of Operation
  - **Mismatch Consideration**
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion

## 8 bits M-2M DACs

## Mismatch Consideration

## Mismatch considerations

- Matching in saturation region is determined by overdrive voltage:

$$\sigma(I_d) = \sqrt{\frac{A_\beta^2}{W \cdot L} + \left(\frac{2 \cdot 100\% \cdot A_{V_{th}}}{V_{ov}}\right)^2 \cdot \frac{1}{W \cdot L}}$$

- Matching of MOS transistors in triode region is affected by output opamp offset:

$$\sigma(I_d) = \sqrt{\frac{A_\beta^2}{W \cdot L} + \left(\frac{100\% \cdot A_{V_{th}}}{V_{ov} - \frac{1}{2}V_{ds}}\right)^2 \cdot \frac{1}{W \cdot L} + \left(100\% \cdot \frac{\Delta V_{ds}}{V_{ds}}\right)^2}$$


# Outline

- 1 8 bits M-2M DAC
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - **Implementation**
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion

# 8 bits M-2M DACs

## Implementation
 
### Schematic diagram of proposed M-2M DAC



- Logic "1" must be equal  $V_{bias}$
- Two modes of operation – current division ( $I_{in} \neq 0$ ) or current source/sink ( $I_{in} = 0$ )
- Transistors can work in various regions of operation
- Simulations results required *special care* – problem with discontinuities of the BSIM transistors model.

# 8 bits M-2M DACs

## Implementation

### Nominal parameters

- $V_{LSB} = 0.5mV$
- $I_{LSB} = 25nA$  ( $R_f = 20k\Omega$ )
- $V_{bias} \simeq 1.2V$  (NMOS) or  $\simeq 1.45V$  (PMOS)
- $V_{ref} \in (1 : 2)V$
- $P_{ladder} \simeq 20\mu W$

### Transistor dimensions

- NMOS Ladder:

$$\frac{W}{L} = \frac{5\mu}{25\mu}$$

- PMOS Ladder:

$$\frac{W}{L} = \frac{7.5\mu}{30\mu}$$

# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion


# 8 bits M-2M DACs

## Design of Output OPAMP – assumptions

### Design goals

- Low offset  $< 5 \text{ mV}$  – **most important**
- Low noise  $< 0.2 \text{ mV}$
- Low power  $< 50 \text{ }\mu\text{W}$
- Output current capability  $> 100 \text{ }\mu\text{A}$

### Low offset diff-amp design

 

$$V_{os} = V_{GS1} - V_{GS2} \approx \sqrt{\sigma_{V_{ThN}}^2 + \frac{I \cdot \sigma_{I_P}^2}{g_{mN}} + \frac{V_{odN}^2 \cdot \sigma_{\beta N}^2}{4}}$$

### Conclusion:

Input pair transistors should have high W/L ratio (high transconductance), however W/L ratio of loading transistors should be low (high overdrive voltage).




# 8 bits M-2M DACs

## Design of Output OPAMP – assumptions

### Design goals

- Low offset  $< 5 \text{ mV}$  – **most important**
- Low noise  $< 0.2 \text{ mV}$
- Low power  $< 50 \text{ }\mu\text{W}$
- Output current capability  $> 100 \text{ }\mu\text{A}$

### Low offset diff-amp design

 

$$V_{os} = V_{GS1} - V_{GS2} \approx \sqrt{\sigma_{V_{ThN}}^2 + \frac{I \cdot \sigma_{I_P}^2}{g_{mN}} + \frac{V_{odN}^2 \cdot \sigma_{\beta N}^2}{4}}$$

### Conclusion:

Input pair transistors should have high W/L ratio (high transconductance), however W/L ratio of loading transistors should be low (high overdrive voltage).


# 8 bits M-2M DACs

## Design of Output OPAMP – assumptions

### Design goals

- Low offset  $< 5 \text{ mV}$  – **most important**
- Low noise  $< 0.2 \text{ mV}$
- Low power  $< 50 \text{ }\mu\text{W}$
- Output current capability  $> 100 \text{ }\mu\text{A}$

### Low offset diff-amp design

 

$$V_{os} = V_{GS1} - V_{GS2} \approx \sqrt{\sigma_{V_{ThN}}^2 + \frac{I \cdot \sigma_{I_P}^2}{g_{mN}} + \frac{V_{odN}^2 \cdot \sigma_{\beta N}^2}{4}}$$

### Conclusion:

Input pair transistors should have high W/L ratio (high transconductance), however W/L ratio of loading transistors should be low (high overdrive voltage).


# 8 bits M-2M DACs

## Design of Output OPAMP – assumptions

### Design goals

- Low offset  $< 5 \text{ mV}$  – **most important**
- Low noise  $< 0.2 \text{ mV}$
- Low power  $< 50 \text{ }\mu\text{W}$
- Output current capability  $> 100 \text{ }\mu\text{A}$

### Low offset diff-amp design

 

$$V_{os} = V_{GS1} - V_{GS2} \approx \sqrt{\sigma_{V_{ThN}}^2 + \frac{I \cdot \sigma_{I_P}^2}{g_{mN}} + \frac{V_{odN}^2 \cdot \sigma_{\beta N}^2}{4}}$$


### Conclusion:

Input pair transistors should have high W/L ratio (high transconductance), however W/L ratio of loading transistors should be low (high overdrive voltage).

# 8 bits M-2M DACs

## Design of Output OPAMP – implementation and results

### Implementation

 


### Simulation results

- Quiescent power = 60.6  $\mu\text{W}$  ( $I_{bias} = 500\text{nA}$ )
- DC Gain (quiescent) = 108.8 dB
- Phase Margin (quiescent) = 72° (10 pF load)
- Input offset ( $1\sigma$ ) = 2 mV
- Noise rms = 105  $\mu\text{V}$  (10 pF load)
- Gain Bandwidth Product = 2.1 MHz (10 pF load)
- Output current capability = 4 mA

# 8 bits M-2M DACs

## Design of Output OPAMP – implementation and results

### Implementation

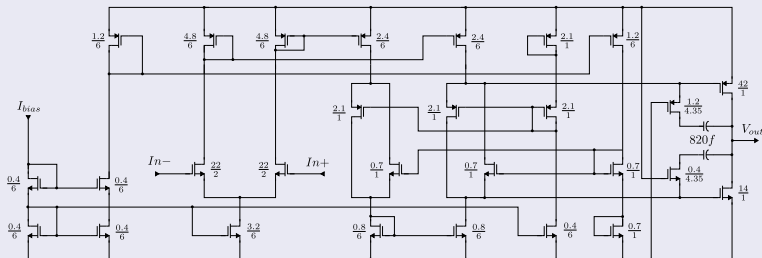


### Simulation results

- Quiescent power =  $60.6 \mu W$  ( $I_{bias} = 500nA$ )
- DC Gain (quiescent) = 108.8 dB
- Phase Margin (quiescent) =  $72^\circ$  (10 pF load)
- Input offset ( $1\sigma$ ) = 2 mV
- Noise rms =  $105 \mu V$  (10 pF load)
- Gain Bandwidth Product = 2.1 MHz (10 pF load)
- Output current capability = 4 mA

# 8 bits M-2M DACs

## Design of Output OPAMP – layout

Layout –  $119 \times 57 \mu\text{m}^2$

 


# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion

# 8 bits M-2M DACs
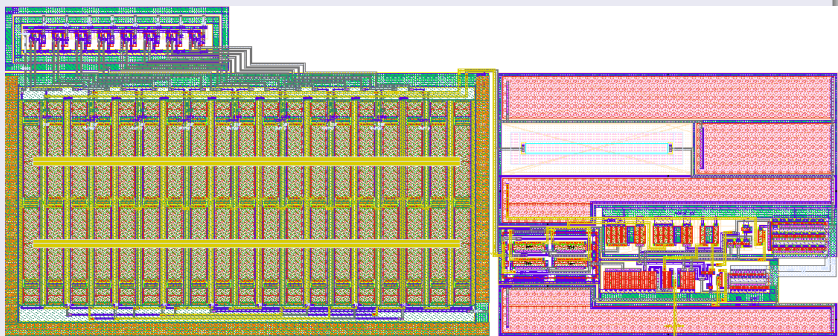
## Layout

NMOS L-2L DAC – core area =  $295 \times 116 \mu\text{m}^2$






# 8 bits M-2M DACs
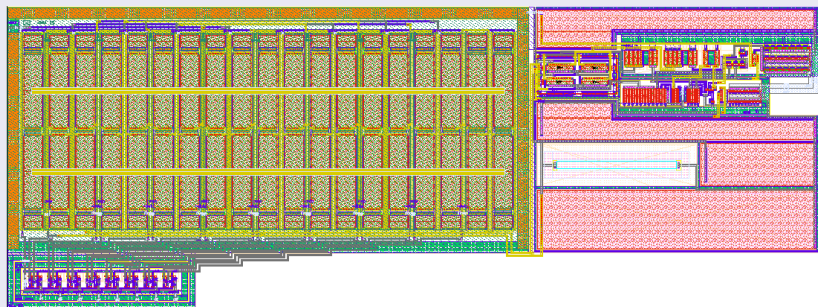
## Layout

PMOS L-2L DAC – core area =  $340 \times 125 \mu\text{m}^2$



# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - Layout
- 3 Conclusion

# Exponential 7-bit DAC

## Idea of circuit

### Goals of design

- Biasing DAC with a few orders of magnitude of output current (power scalling)
- Relatively low area and number of bits
- About 10 % of increment step

Proposition – exponential transfer function, with 8.5% increment and 7 bits resolution

Input	Output current [ $I_{LSB}$ ]
0	1
1	1.09
...	...
15	3.58
16	3.90
...	...
127	48 776.31

# Exponential 7-bit DAC

## Idea of circuit

### Goals of design

- Biasing DAC with a few orders of magnitude of output current (power scalling)
- Relatively low area and number of bits
- About 10 % of increment step

Proposition – exponential transfer function, with 8.5% increment and 7 bits resolution

Input	Output current [ $I_{LSB}$ ]
0	1
1	1.09
...	...
15	3.58
16	3.90
...	...
127	48 776.31

# Exponential 7-bit DAC Implementation

## Solution – 8 4-bits subDACs


Input	Ideal weights	Implemented weights	Mismatch (%)
0	1	1	0
1	1.09	1.1	1.04
2	1.19	1.2	1.24
3	1.29	1.3	0.74
4	1.40	1.45	3.21
5	1.53	1.6	4.6
6	1.67	1.75	5.09
7	1.81	1.9	4.8
8	1.97	2.1	6.39
9	2.15	2.3	7.03
10	2.34	2.5	6.85
11	2.55	2.7	6
12	2.77	2.95	6.38
13	3.02	3.2	5.99
14	3.29	3.45	4.96
15	3.58	3.7	3.39
0 (next stage)	3.90	4	2.66

# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - **Implementation**
  - Simulation results
  - Layout
- 3 Conclusion

# Exponential 7-bit DAC Implementation

## Block diagram of Exp-DAC

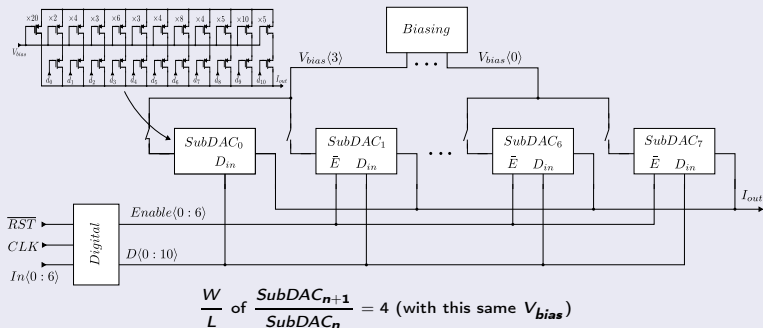


## Dimensions of SubDACs Current Sources

SubDAC No	0	1	2	3	4	5	6	7
Unit CS $\frac{W}{L}$	$\frac{0.4}{28}$	$\frac{0.4}{7.5}$	$\frac{0.4}{28}$	$\frac{0.4}{7}$	$\frac{0.7}{7.5}$	$\frac{1.4}{3.75}$	$\frac{0.8}{5}$	$\frac{1.6}{2.5}$

# Exponential 7-bit DAC Implementation

## Schematic of biasing circuit

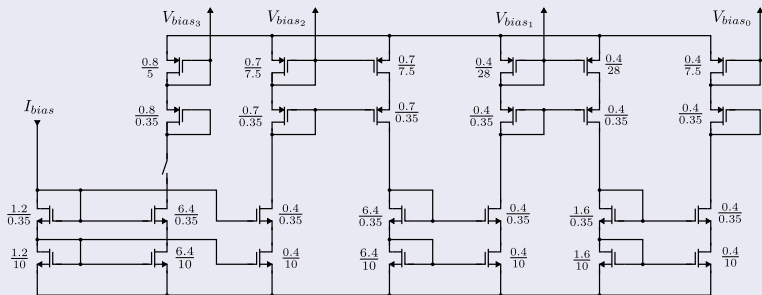

Branch	$I_{bias}$	$V_{bias_3}$	$V_{bias_2}$	$V_{bias_1}$	$V_{bias_0}$
Current	100 nA	533 nA	33.3 nA	2.1 nA	516 pA




# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - **Simulation results**
  - Layout
- 3 Conclusion

# Exponential 7-bit DAC

## Simulation results – DC


### DC characteristic

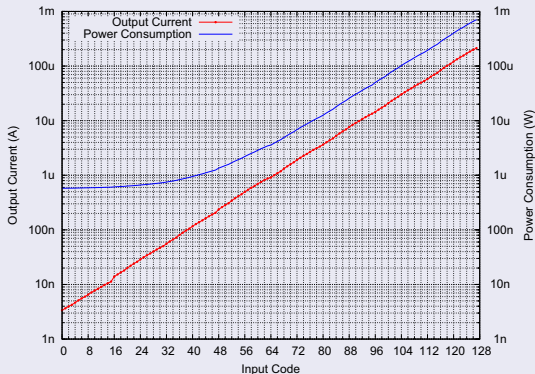


# Exponential 7-bit DAC

## Simulation results – Monte Carlo Worst Cases

### Monte Carlo & Worst Cases

 

Monte Carlo

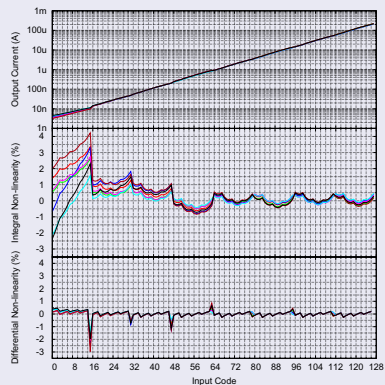

Worst Cases


# Outline

- 1 8 bits M-2M DACs
  - Goals of Design
  - Principle of Operation
  - Mismatch Consideration
  - Implementation
  - Design of Output OPAMP
  - Layout
- 2 Exponential 7-bit DAC
  - Idea
  - Implementation
  - Simulation results
  - **Layout**
- 3 Conclusion

# Exponential 7-bit DAC

## Layout

Core area  $725 \times 93 \mu\text{m}$

 

# Conclusion

## M-2M DAC

- M-2M ladder seems to be promising Low-power and Small-area DAC architecture.
- Offset of output OPAMP is main resolution limitation for ladder working in triode region.
- Simulation results should be done using EKV MOS model – usually not delivered with the technology.
- The measurements tell us the truth

## Exp DAC

- The 7-bits DAC with exponential transfer function is designed.
- 5 order of magnitude of output current with similar area to linear DAC.
- Used as biasing circuit should be ideally for ASICs with aggressive power scaling.

# Conclusion

## M-2M DAC

- M-2M ladder seems to be promising Low-power and Small-area DAC architecture.
- Offset of output OPAMP is main resolution limitation for ladder working in triode region.
- Simulation results should be done using EKV MOS model – usually not delivered with the technology.
- The measurements tell us the truth

## Exp DAC

- The 7-bits DAC with exponential transfer function is designed.
- 5 order of magnitude of output current with similar area to linear DAC.
- Used as biasing circuit should be ideally for ASICs with aggressive power scaling.