

AGH UNIVERSITY OF SCIENCE AND TECHNOLOGY



## SALT ver3 1<sup>st</sup> measurements

Marek Idzik on behalf of AGH-UST

Faculty of Physics and Applied Computer Science AGH University of Science and Technology

SALT 18/02/2019



#### SALT v3 18/2/2019 Measurements of side channels -1,128 Setup

#### **Default settings:**


Preamp. Current 15 (0F) Shaper current 12 (0C) S2Diff current 12 (0C) Calib. Pulse 12 (0C) VCM DAC 32 (20) TrimDAC 128 (80) ADC delay 2 (2)

In addition: Monitoring ADCs OFF Test Channel ADCs OFF Measurements in next slides were done for analog and digital grounds shorted on PCB in ONLY ONE place GND\_join3

Later on we have shorted ALL FOUR GND\_joins but we have not seen significant differences

#### SALT v3 18/2/2019 NO Sensor Channel 128, Vpp/baseline vs no. ADCs ON

AGH

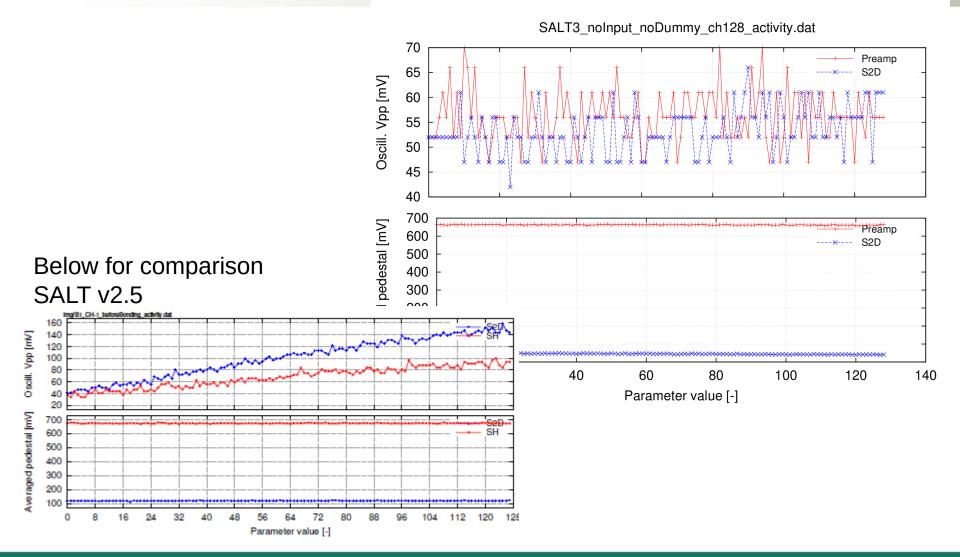




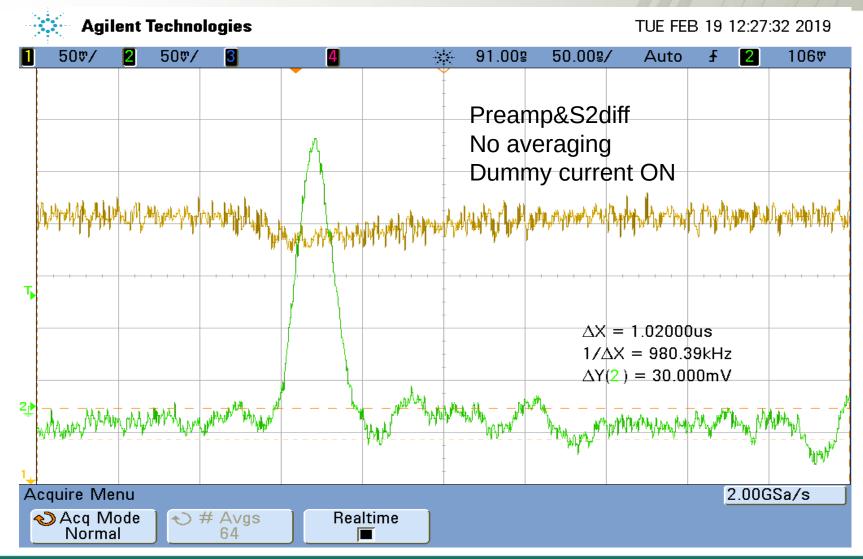
## SALT v3 19/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Vdda quality











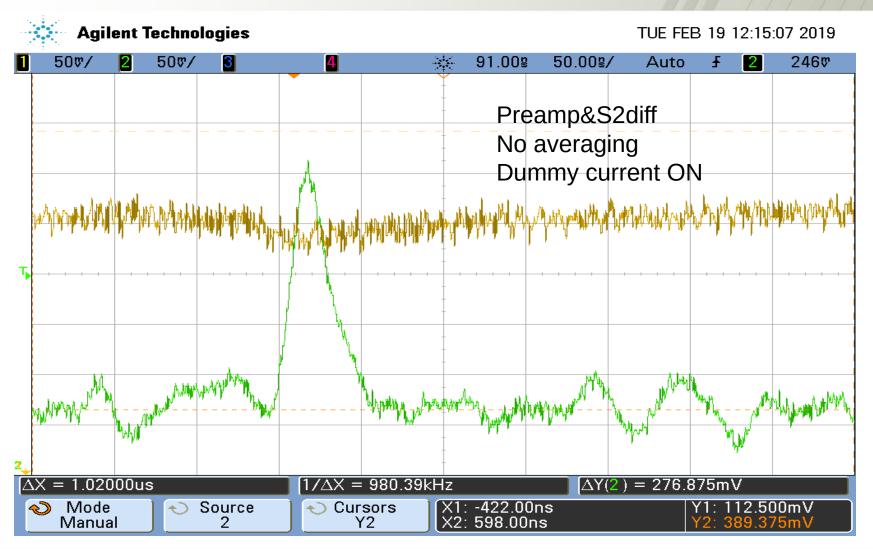




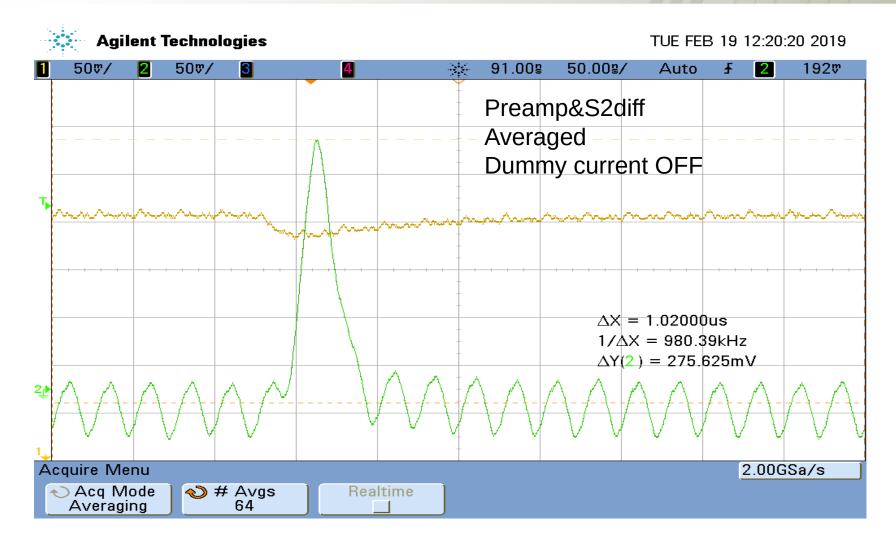




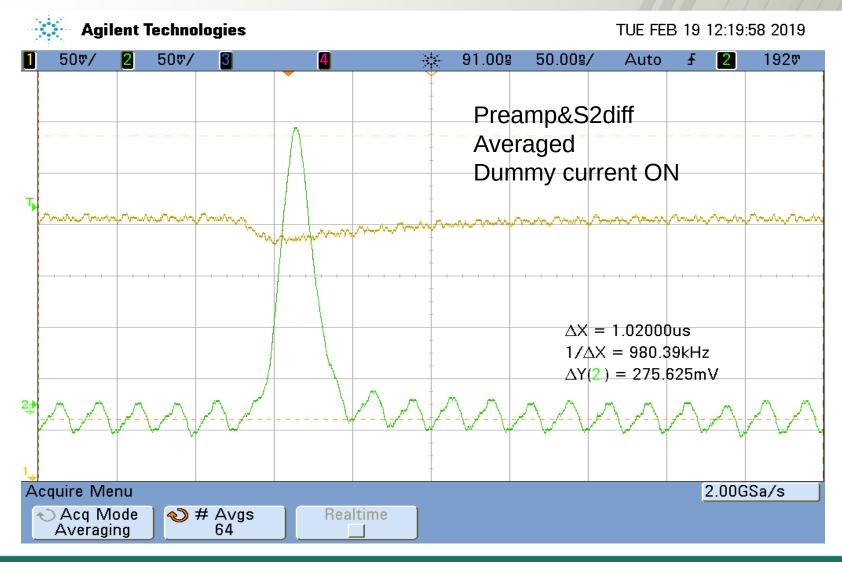




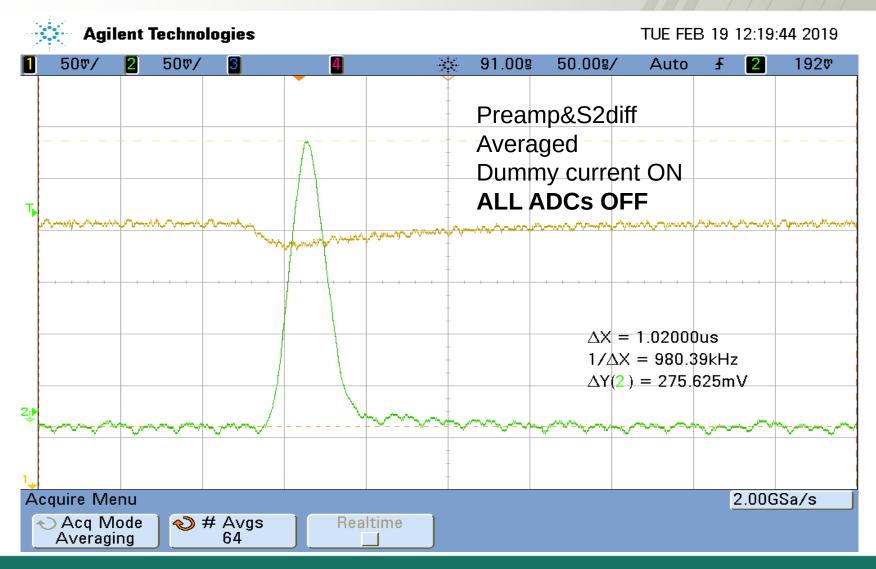




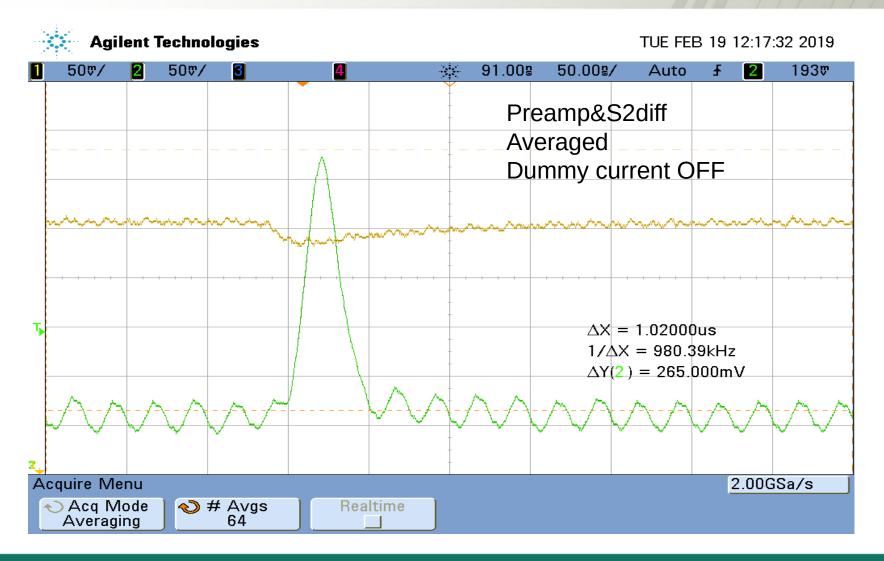



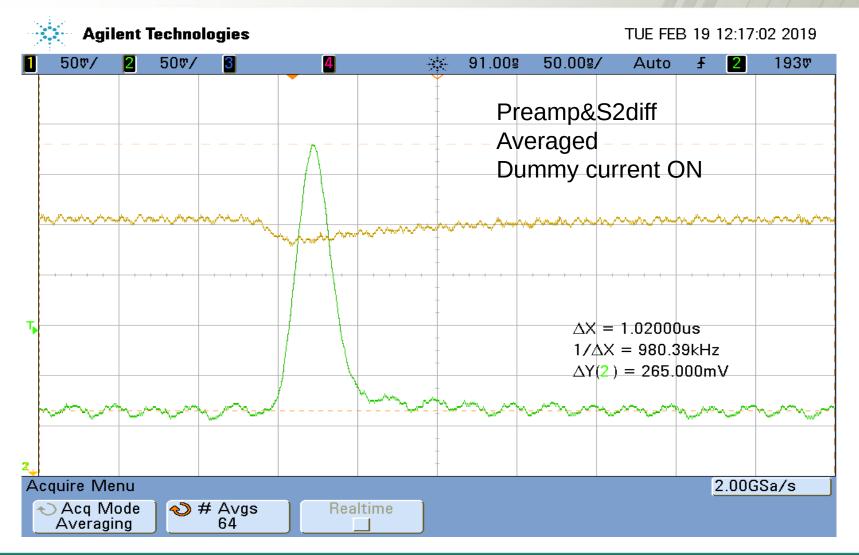




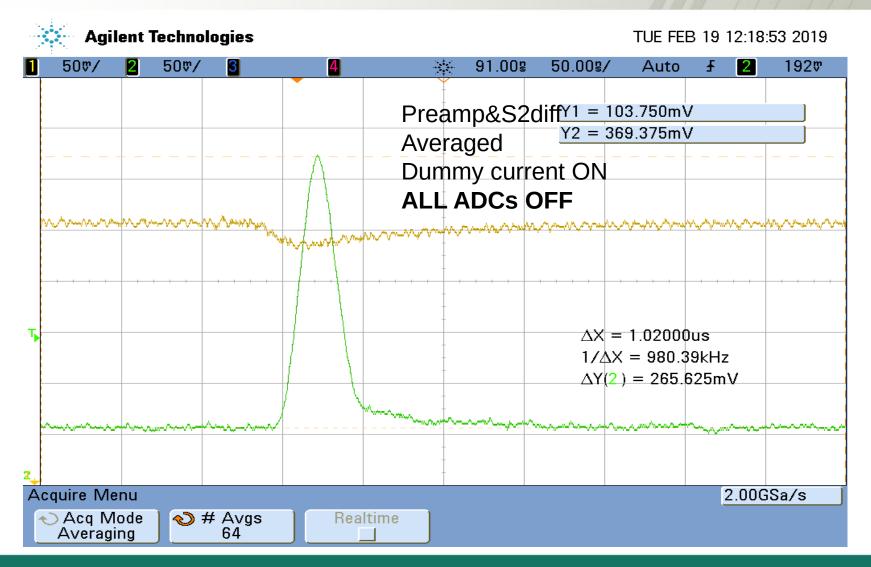


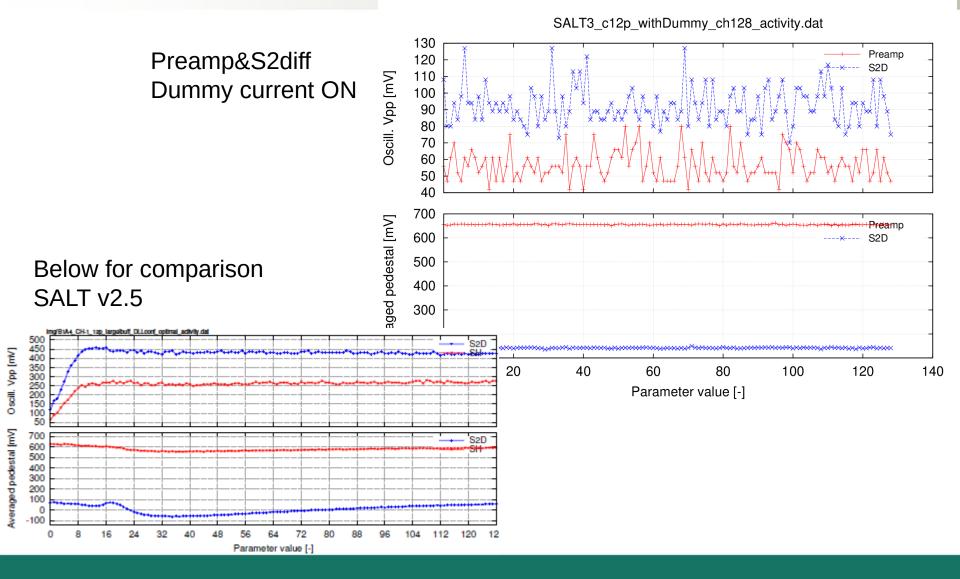
#### SALT v3 19/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, Vpp/baseline vs no. ADCs ON





## SALT v3 20/2/2019 Measurements of side channels -1,128 Setup

#### From now on we have shorted ALL FOUR GND\_joins We have also switched ON ALL ADCs (also test channels and monitors ones)


From now on:

- the "noise" Vpp is NOT done with instant values but it is taken from AVERAGE
- it was done to suppress the noise and to see only synchronous disturbances



### SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel -1, Vpp/baseline vs no. ADCs ON

#### Preamp&S2diff

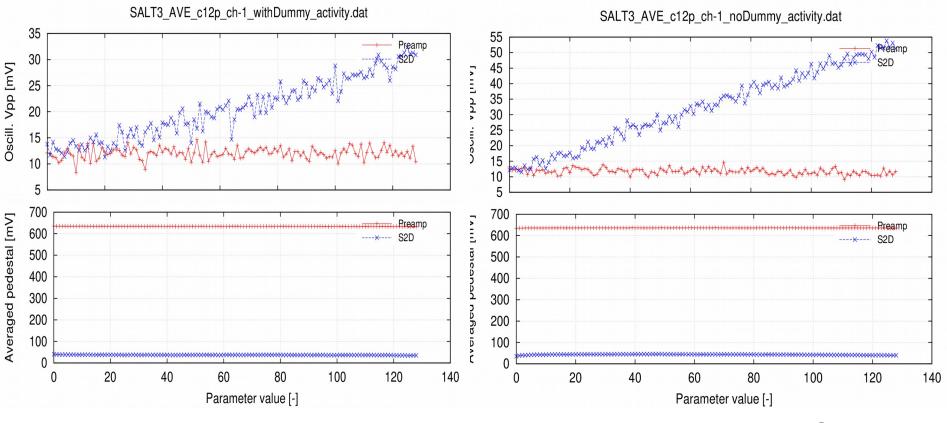


Dummy current ON

Dummy current OFF



#### SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel -1, Vpp/baseline vs Vcm DAC

# Preamp&S2diff VcmDAC default=32!

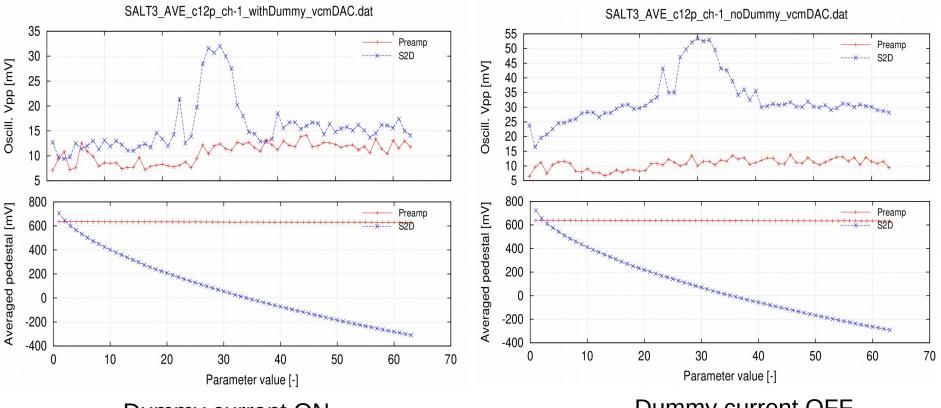


Dummy current ON

Dummy current OFF




### SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, Vpp/baseline vs Vcm DAC


#### Preamp&S2diff VcmDAC default=32!

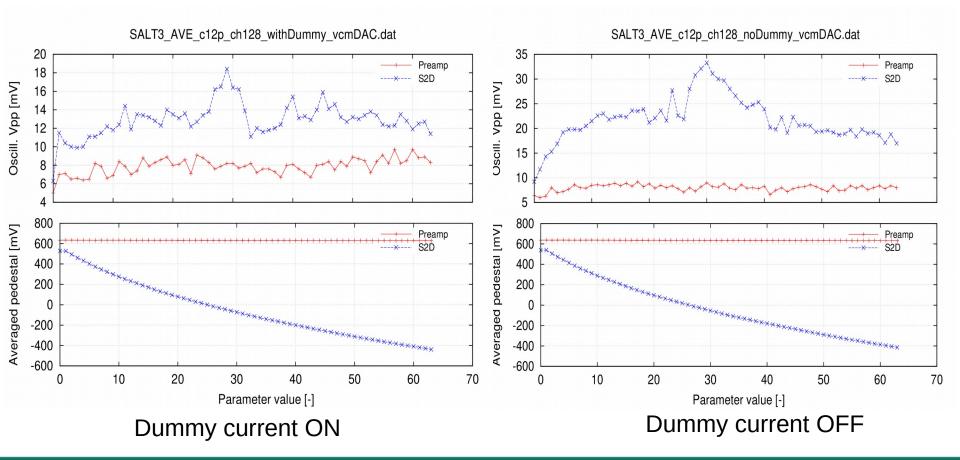




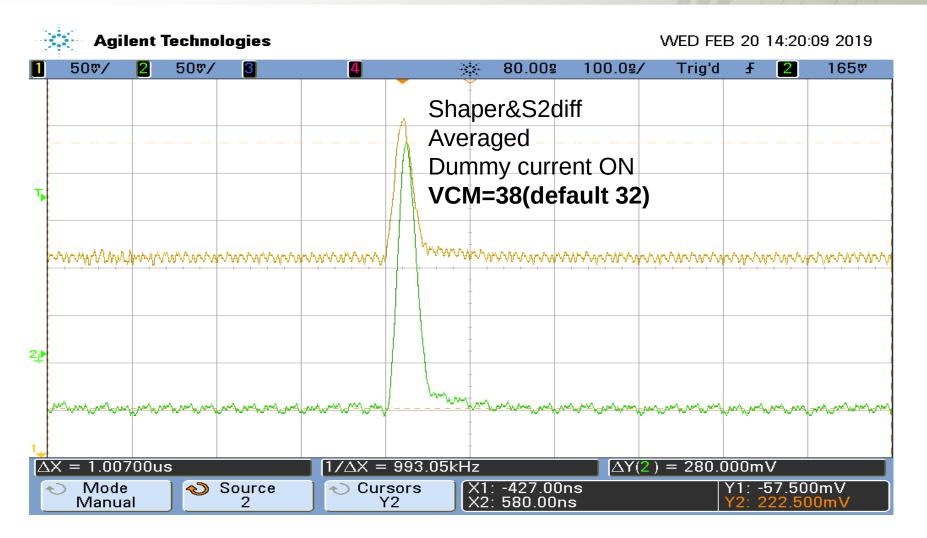




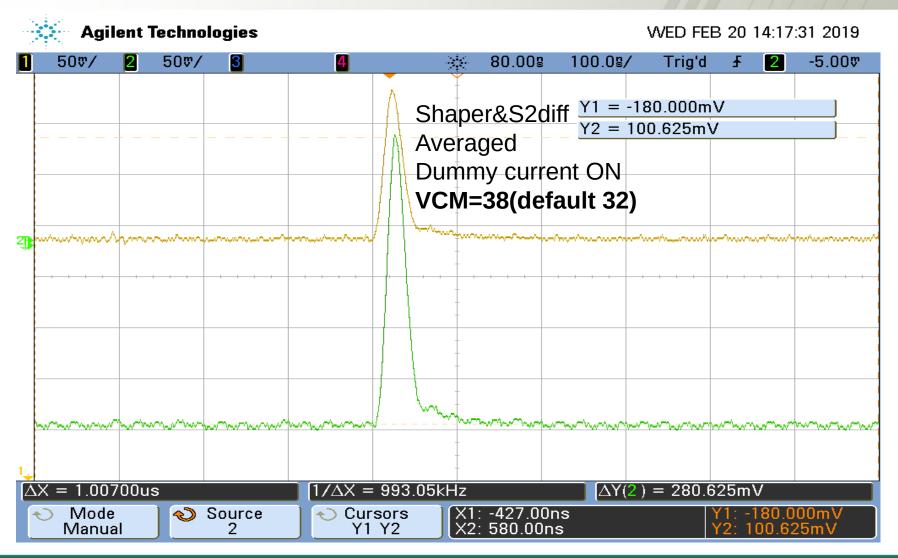




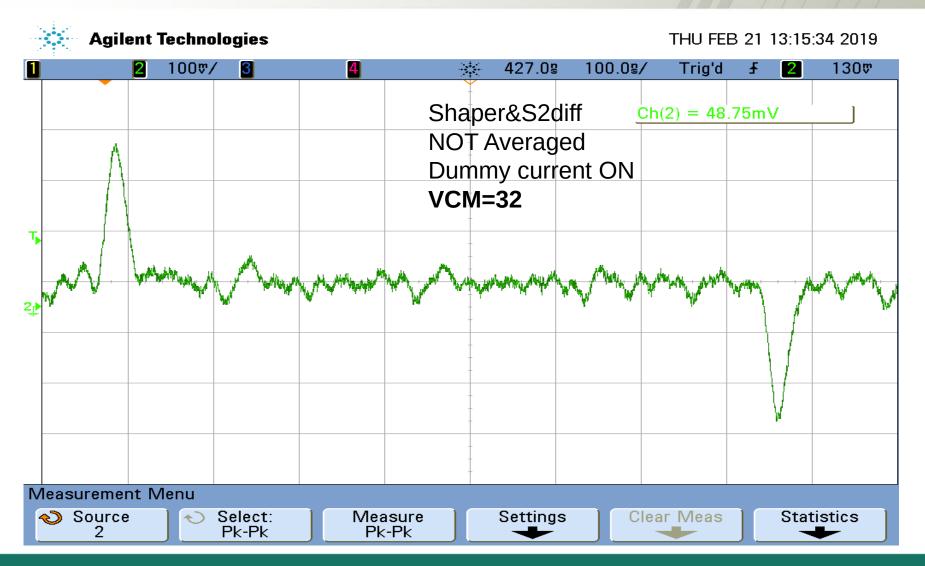




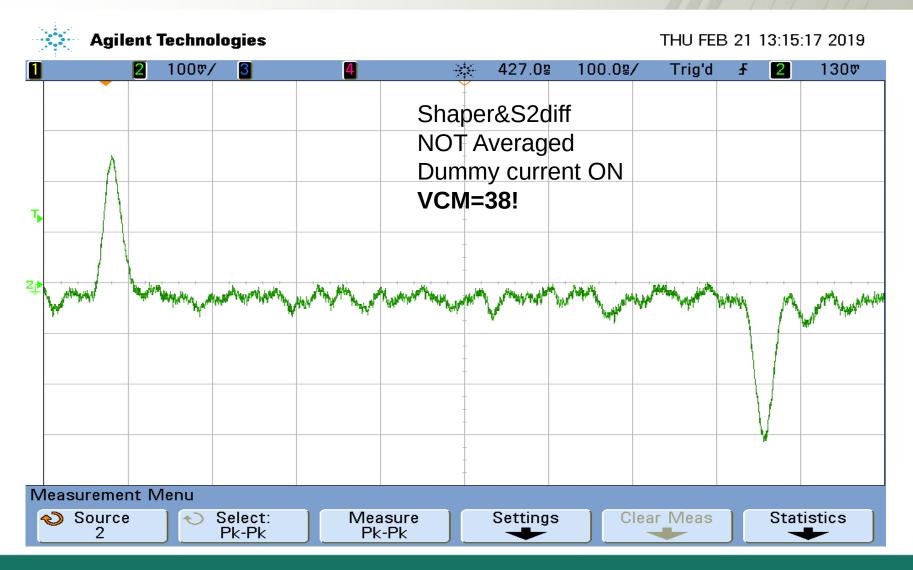




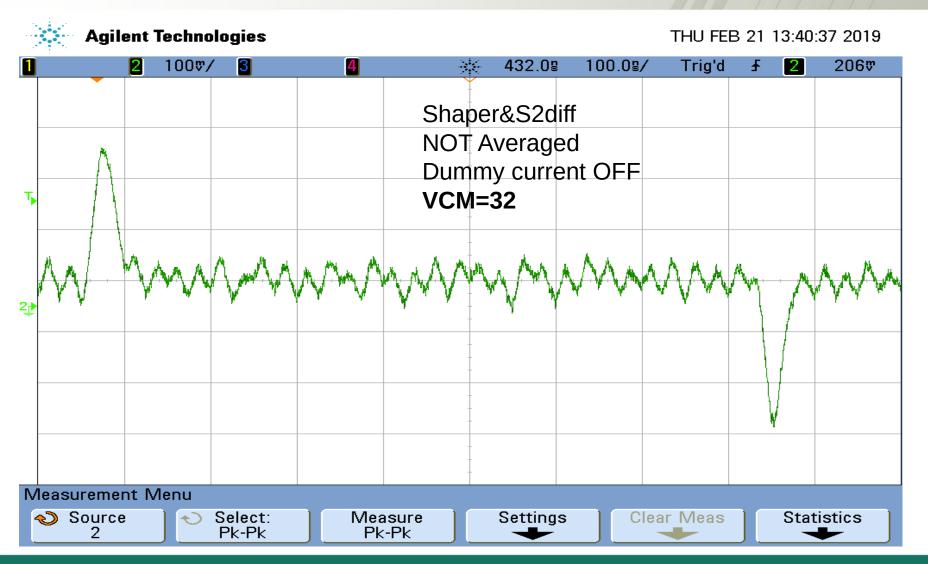




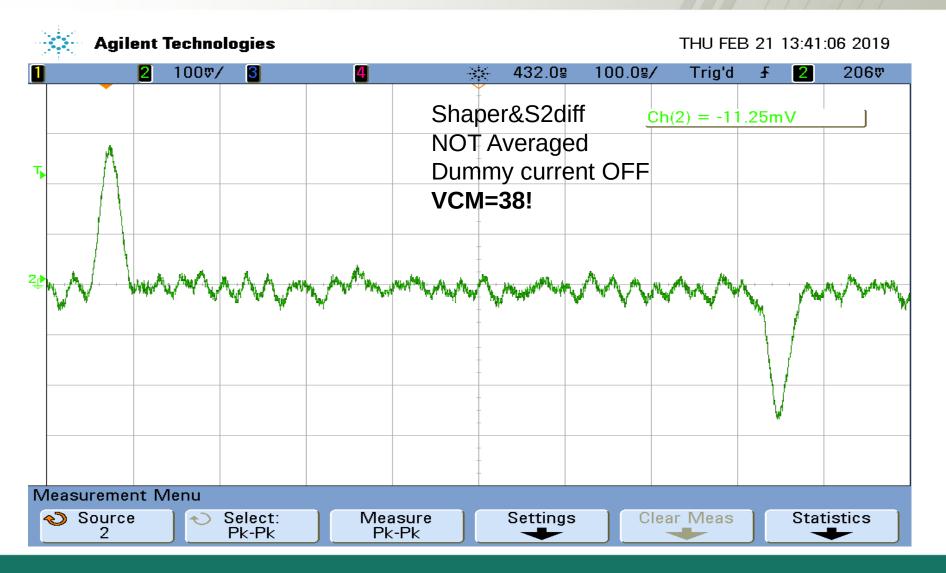




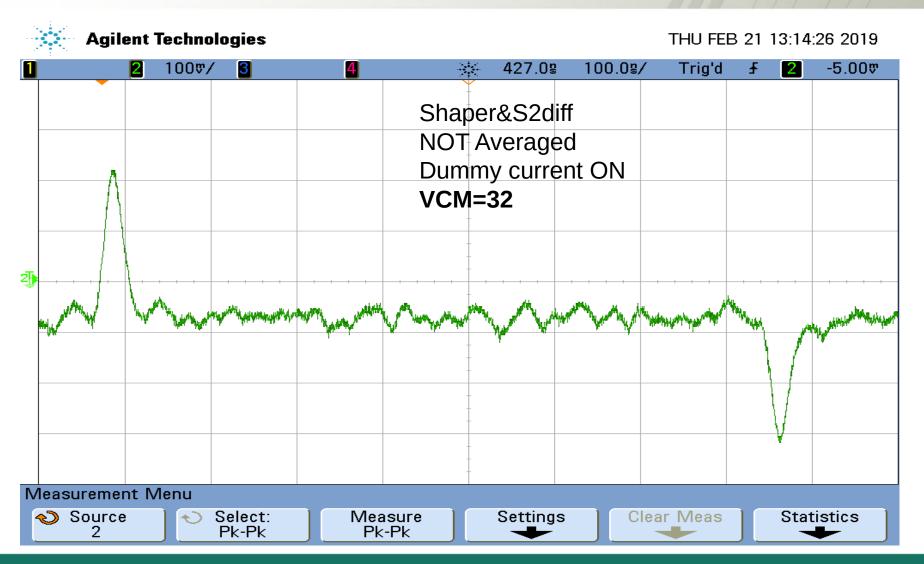




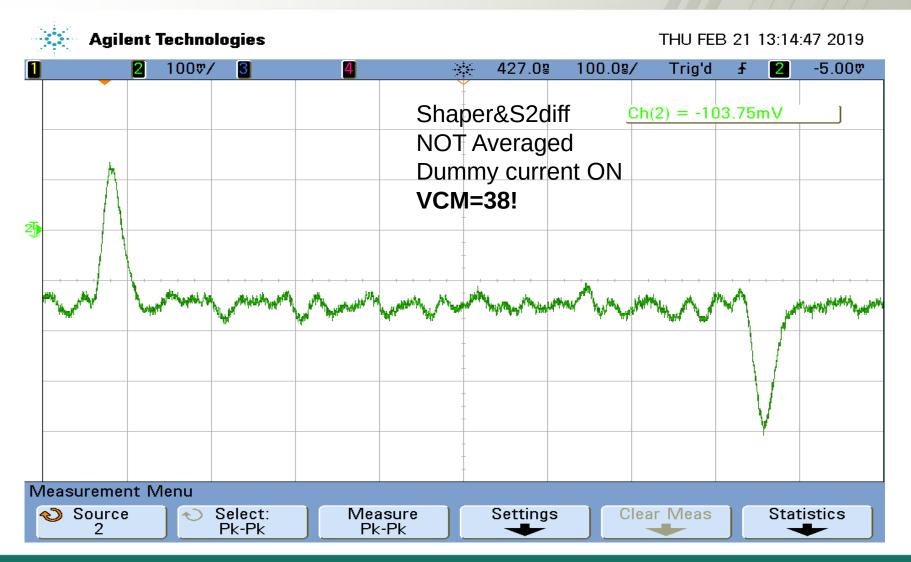



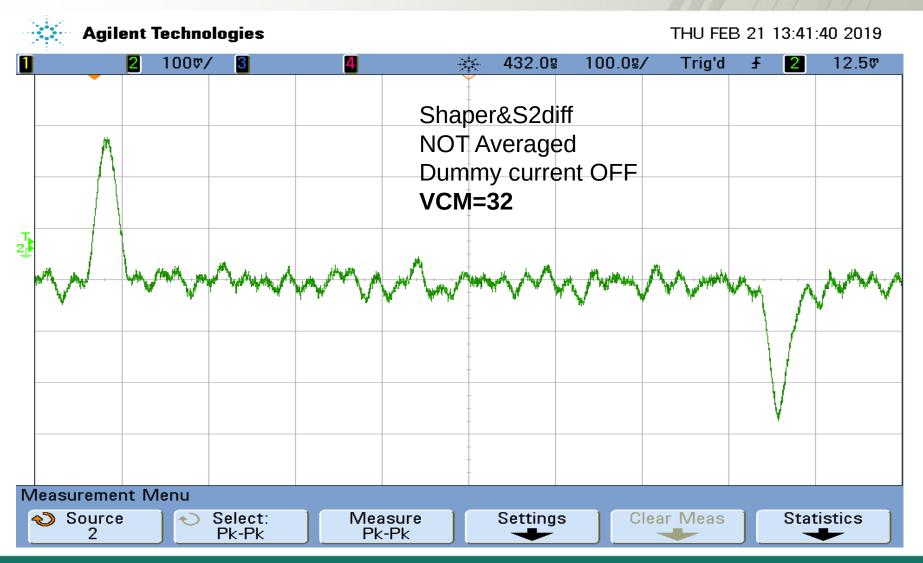




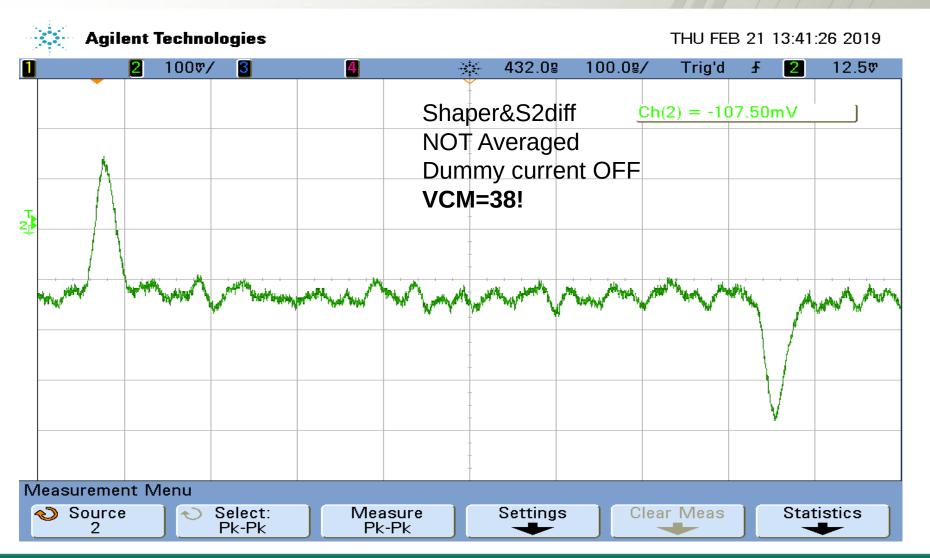



#### SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel -1, Vpp/baseline vs Preamp DAC

## Preamp&S2diff PreampDAC default=15!

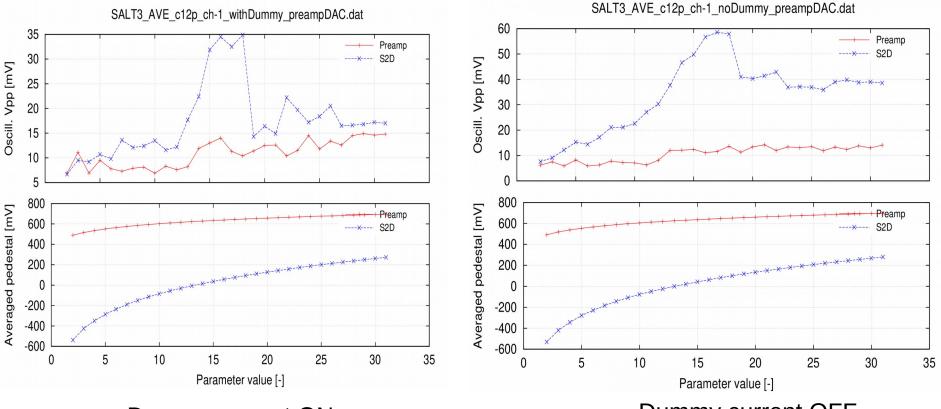


Dummy current ON

Dummy current OFF



## SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, Vpp/baseline vs Preamp DAC


# Preamp&S2diff PreampDAC default=15!

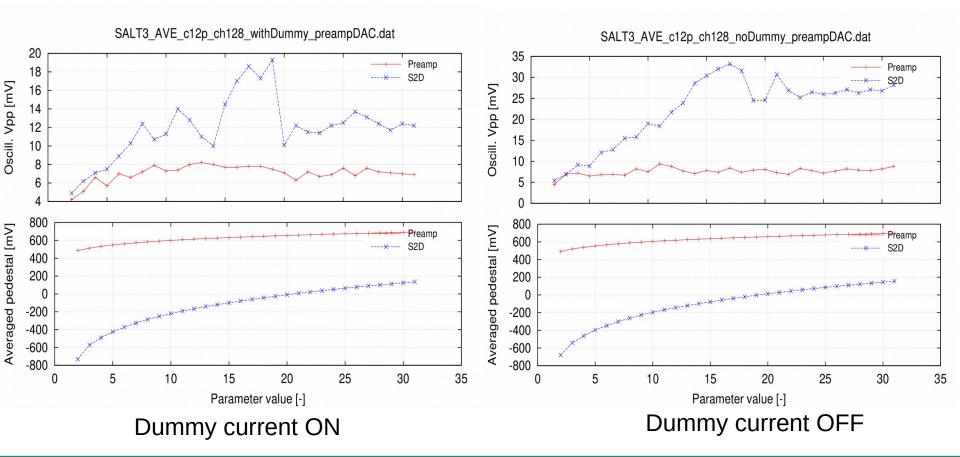



#### SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel -1, Vpp/baseline vs Shaper DAC

#### Preamp&S2diff ShaperDAC default=12

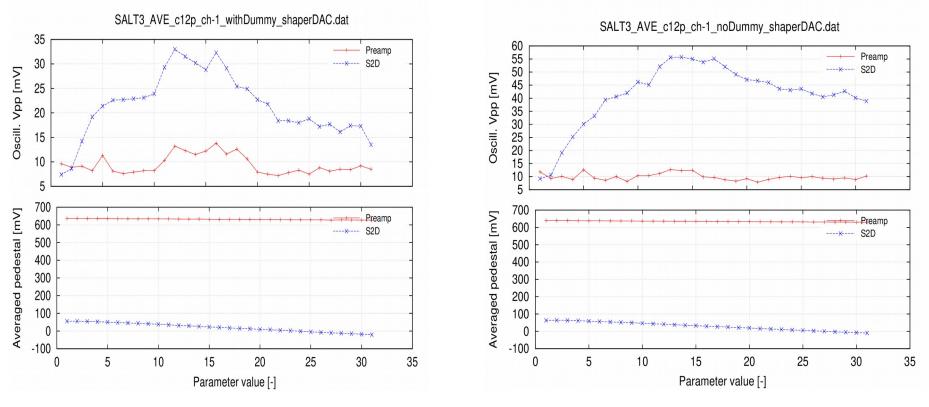


Dummy current ON

Dummy current OFF



#### SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel -1, Vpp/baseline vs S2Diff DAC

#### Preamp&S2diff S2DiffDAC default=12

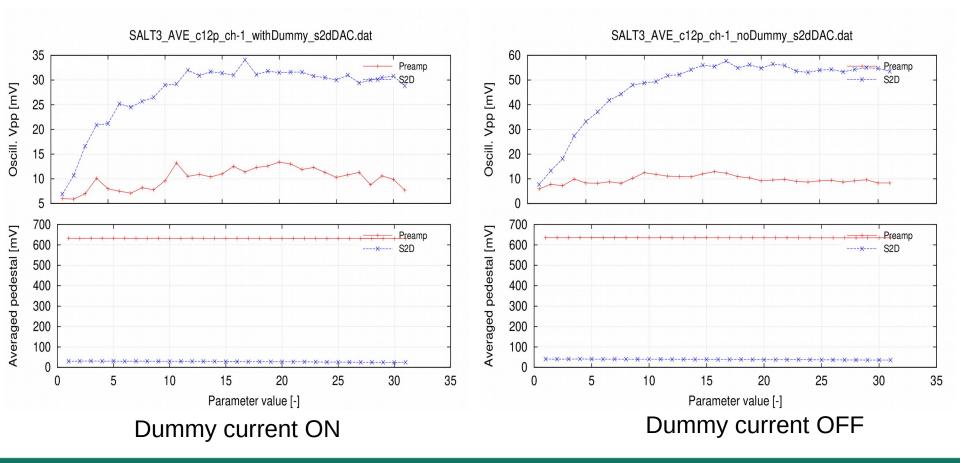




## SALT v3 20/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel -1, Vpp/baseline vs other DACs

In addition, the dependence on CalibDAC and on ADCdelayDAC was measured. Flat curves (No dependence) were obtained.



#### SALT v3 22/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, SNR vs no. ADCs ON
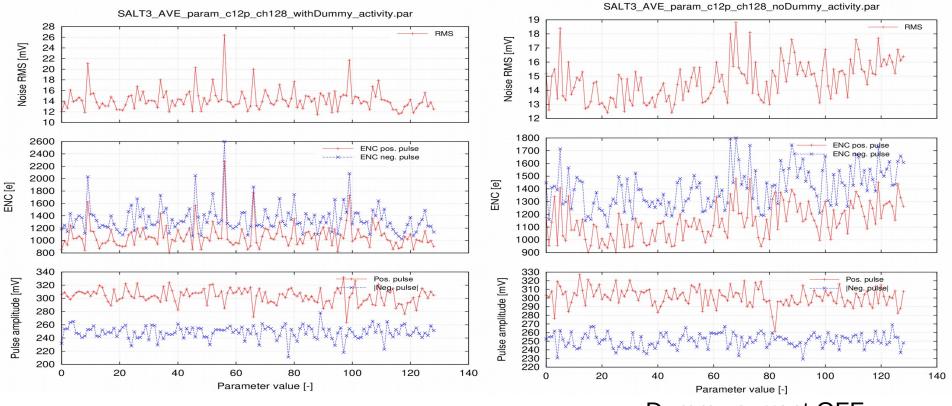
## Noise RMS, ENC, Pulse amplitude **All ADCs ON default**




Dummy current ON

Dummy current OFF



#### SALT v3 22/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, SNR vs Vcm DAC

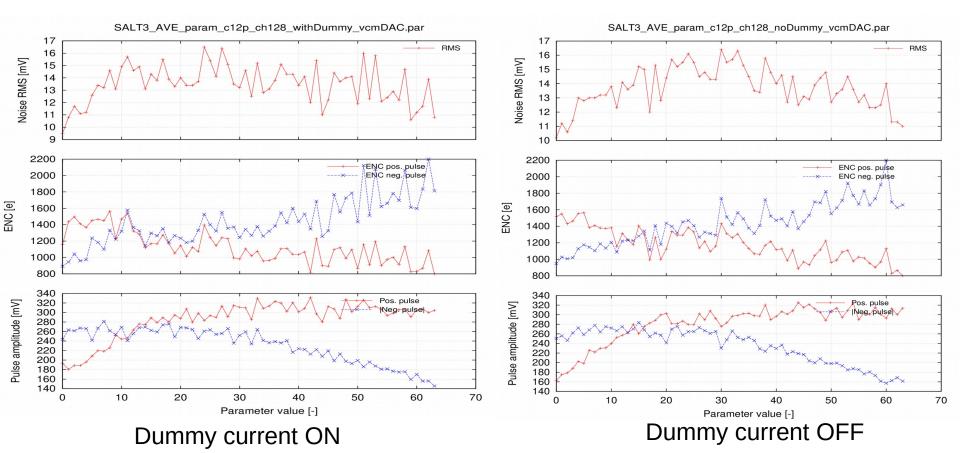
## Noise RMS, ENC, Pulse amplitude VcmDAC default=32





#### SALT v3 22/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, SNR vs Preamp DAC

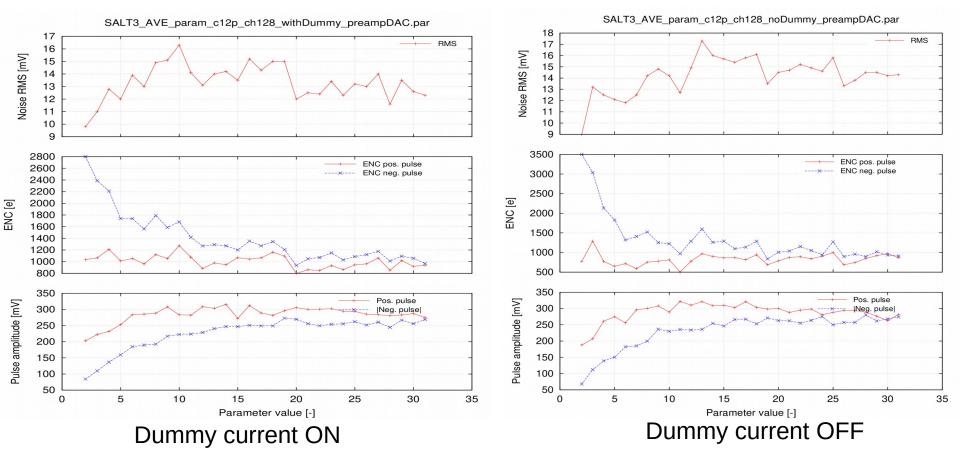
#### Noise RMS, ENC, Pulse amplitude PreampDAC default=15





#### SALT v3 22/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, SNR vs S2Diff DAC
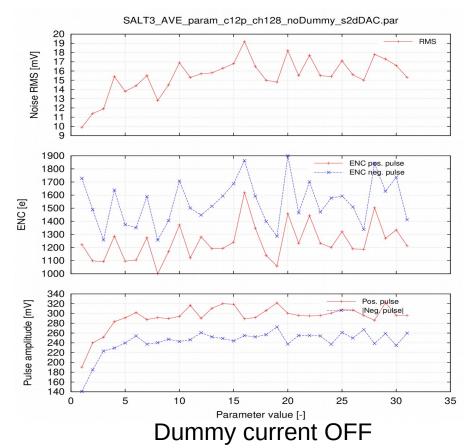
## Noise RMS, ENC, Pulse amplitude S2DiffDAC default=12




Dummy current ON



#### SALT v3 22/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, SNR vs ADC delay

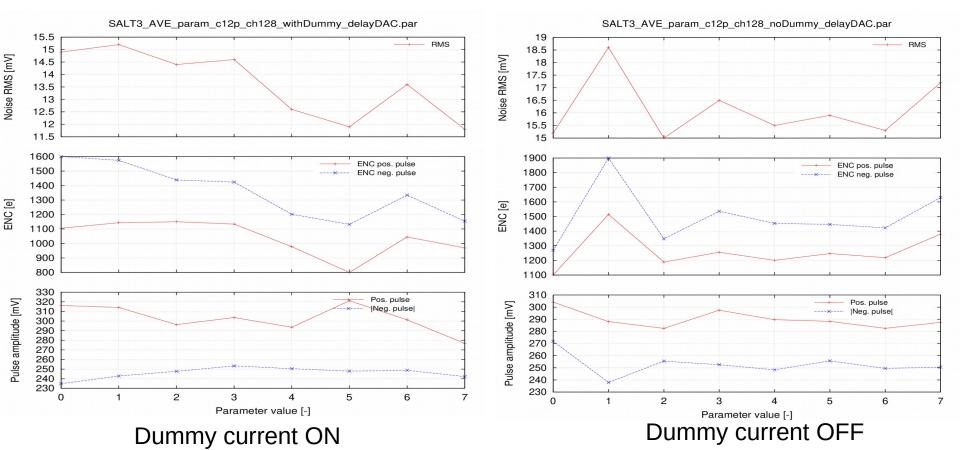
# Noise RMS, ENC, Pulse amplitude **ADC delay default=2**





#### SALT v3 22/2/2019 Sensor 12pF+1-3pFparas. on chan. -1,128 Channel 128, S2Diff Amp. vs Calib DAC


#### Pulse amplitude

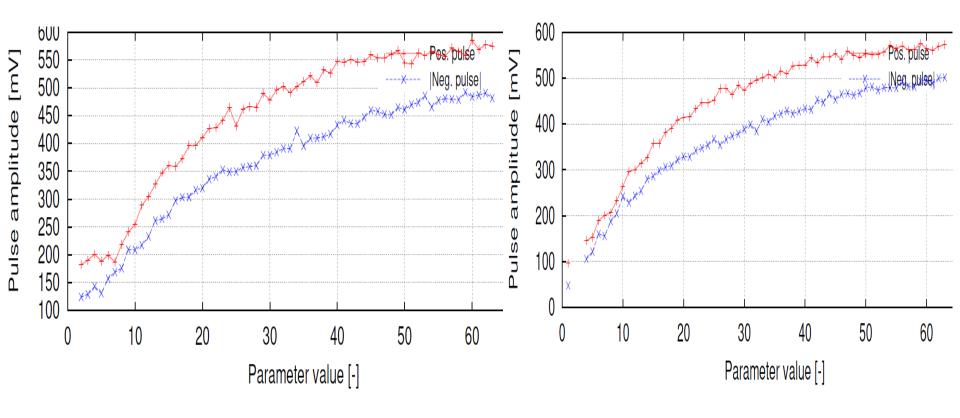


Dummy current ON

Dummy current OFF




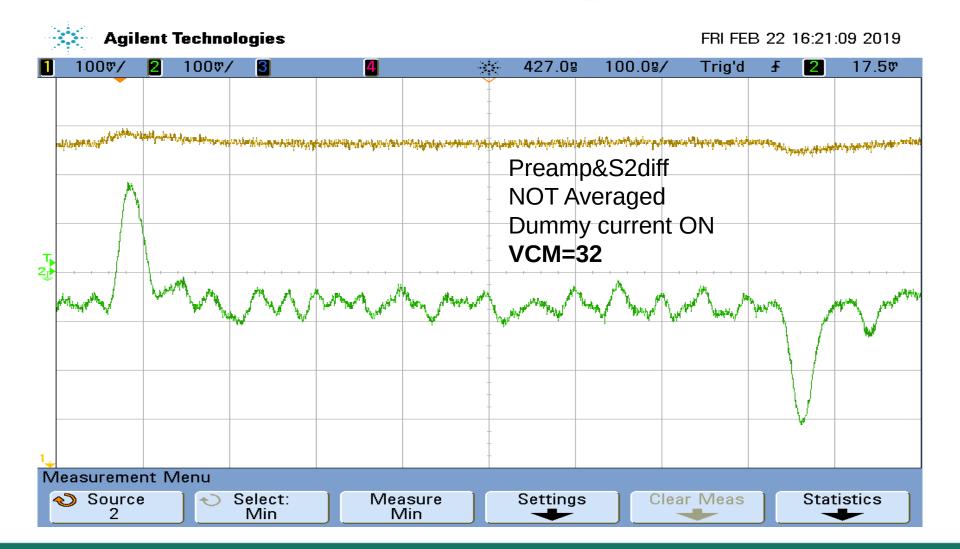




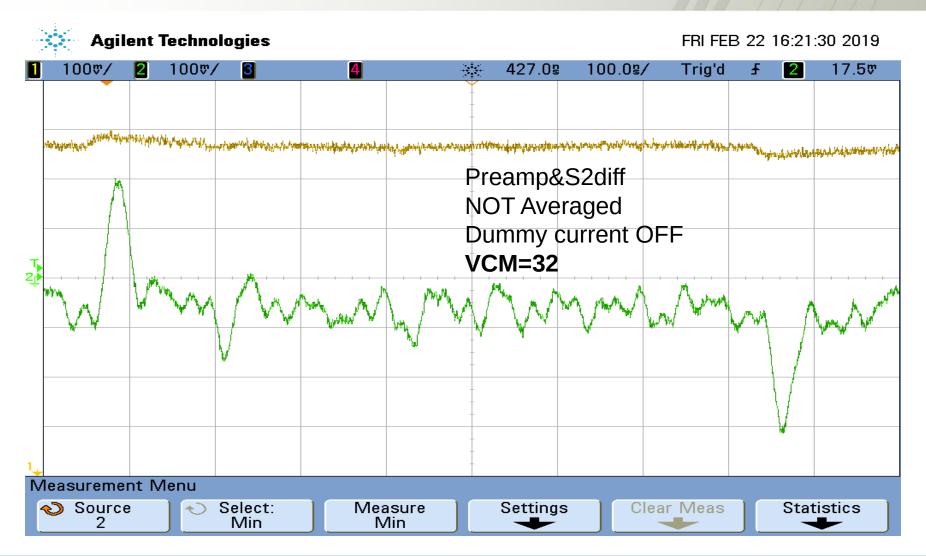



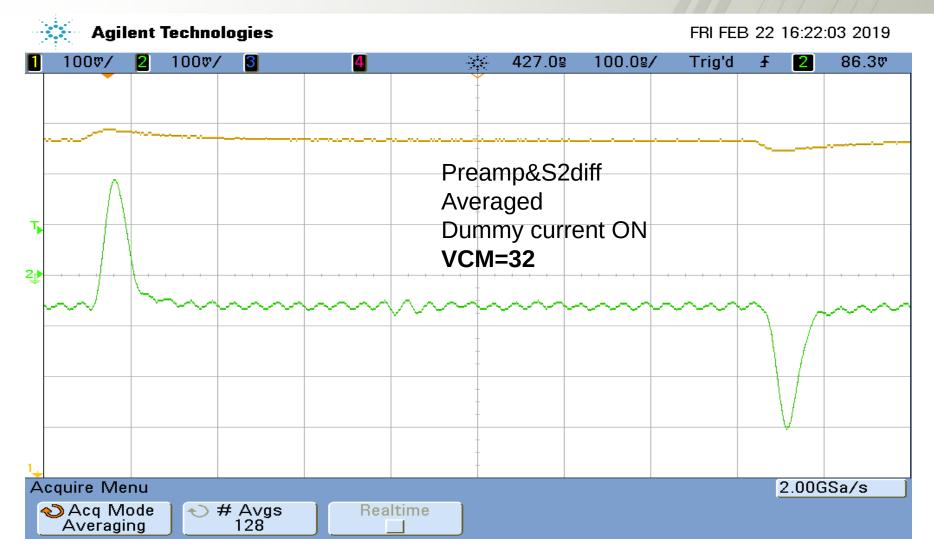



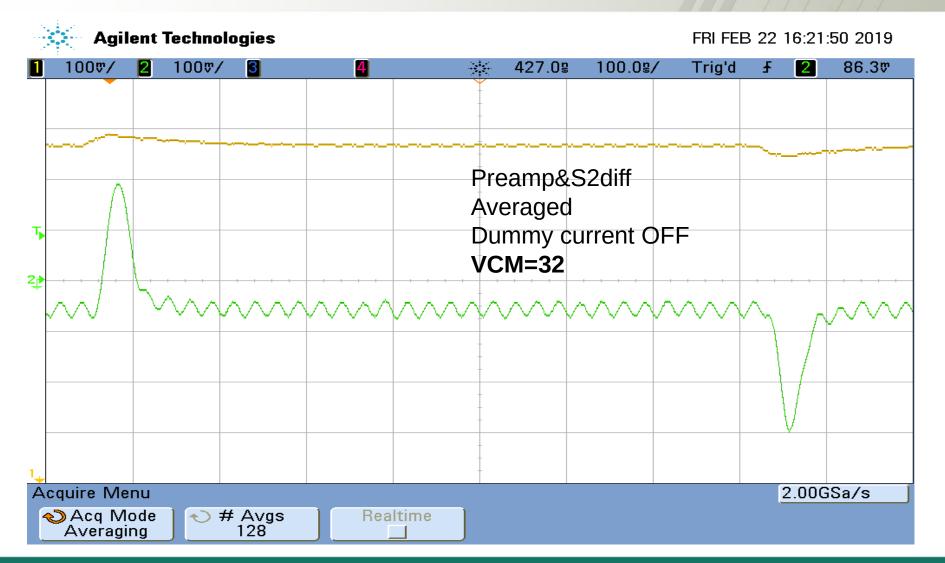




Measurements were done with all parameters set with defaults values (slide2). Dummy current is ON and 128 ADCs are ON Default HV=200V For sensor decoupling resistor RHV4 **SHORTED** 

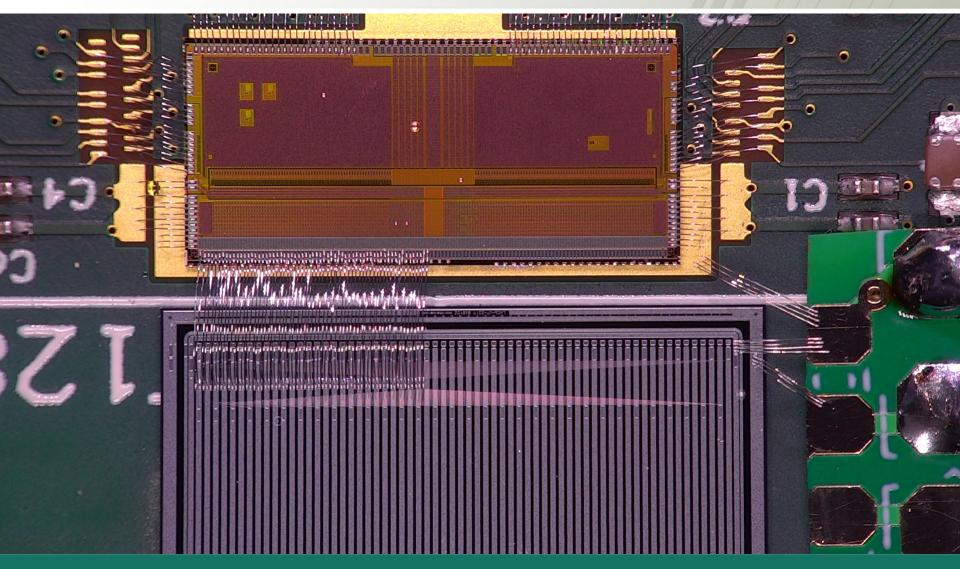Measurements without sensor were also done (not shown here) giving good results Important difference – effect of VcmDAC practically not observed on this chip/board









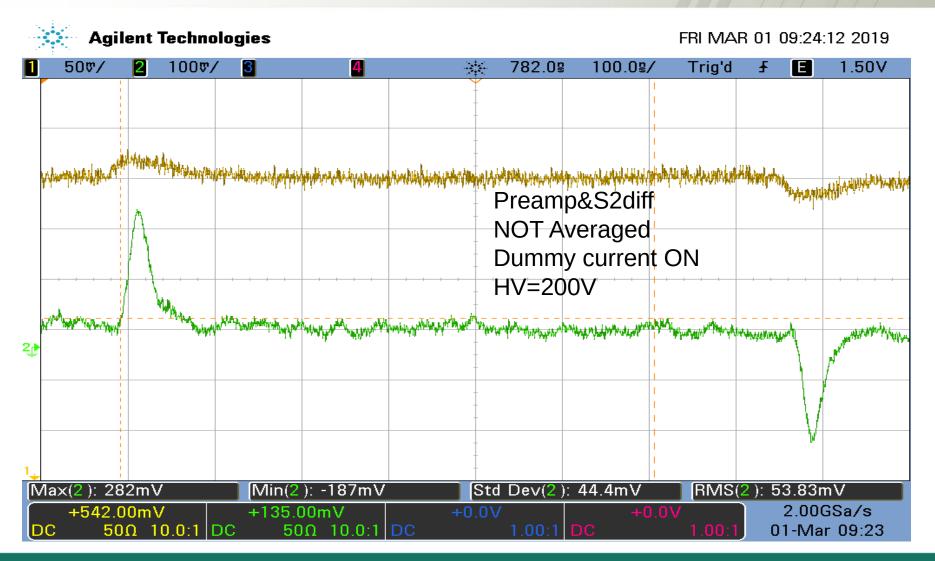Please DO NOT look at RHV1-4 status, because later on we did various tries. Results in next slides were obtained with RHV4 SHORTED. RHV1-3 were 1KOhm.








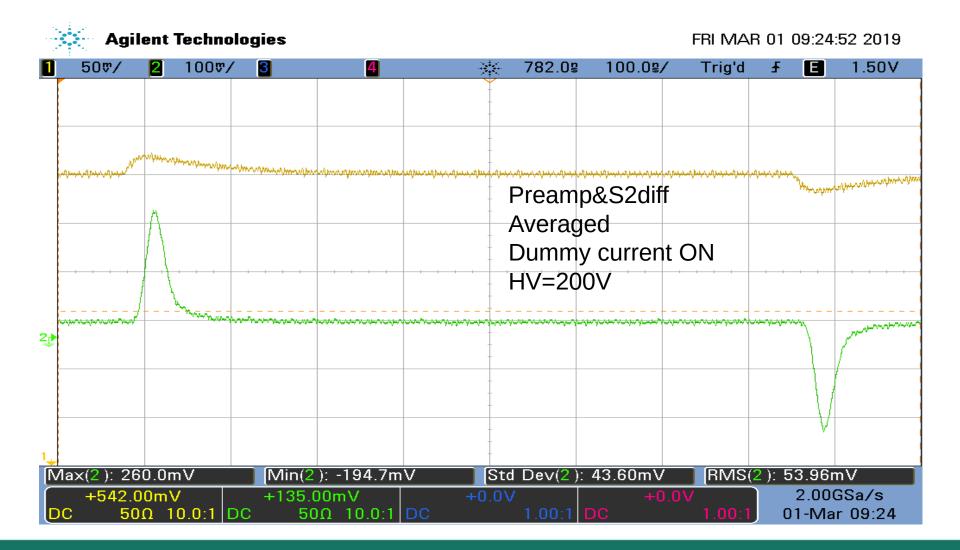



#### SALT v3 2<sup>nd</sup> board 1/3/2019 Real Sensor "baby2" added Channel -1, SNR vs no. of ADCs ON

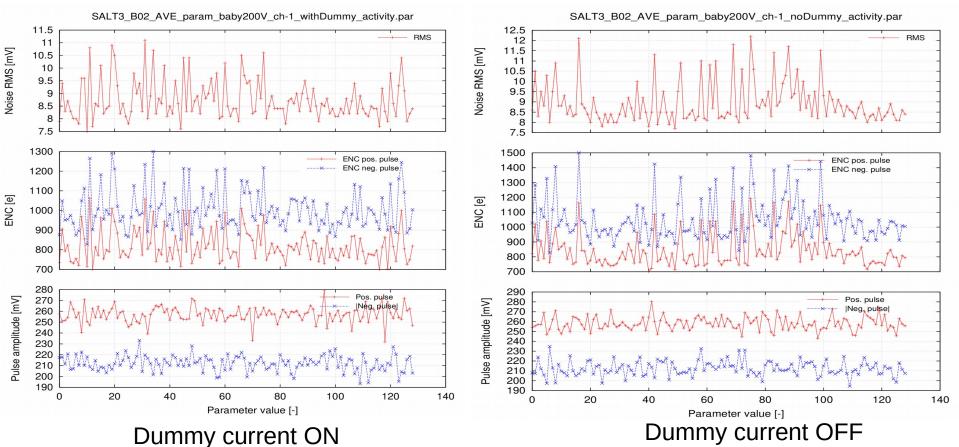
# Noise RMS, ENC, Pulse amplitude All ADCs ON default





#### SALT v3, 2<sup>nd</sup> board 1/3/2019 Real Sensor "baby2" added Channel -1, SNR vs Vcm DAC
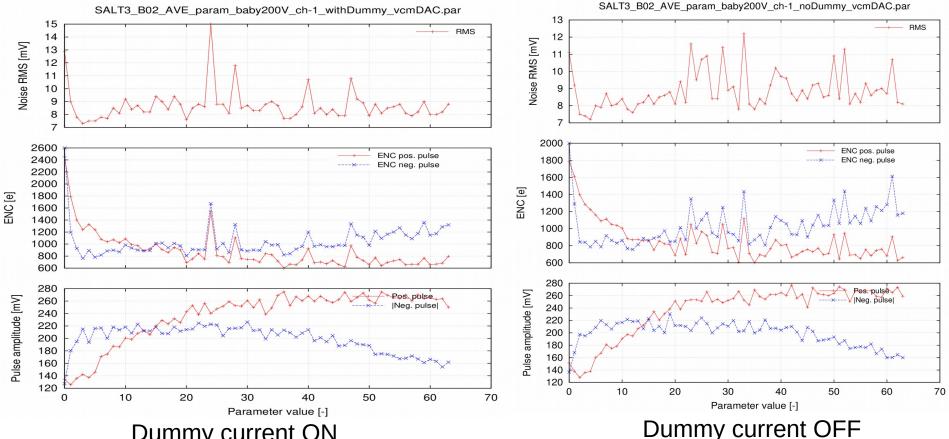
#### Noise RMS, ENC, Pulse amplitude VcmDAC default = 32



Dummy current ON



